

# Sequential Logic

Jinyang Li

# What we've learnt so far

- Combinatorial logic
  - E.g. Multiplexors (Mux), Decoders
  - Two ways of building a CL
    - Truth table  $\rightarrow$  sum of products circuits
    - ROM
- ALU
  - Compute all operations (+, OR, AND, NOR), multiplexer picks the result
  - Building a 64-bit adder
    - Ripple carry chains together 1-bit adders
    - Carry lookahead




Not yet covered

# Today's lesson plan

- Ripple carry vs. Carry lookahead
- Sequential circuit: Memory (state) elements
- Sequential circuit: Finite State Machine

# Downside of ripple carry?

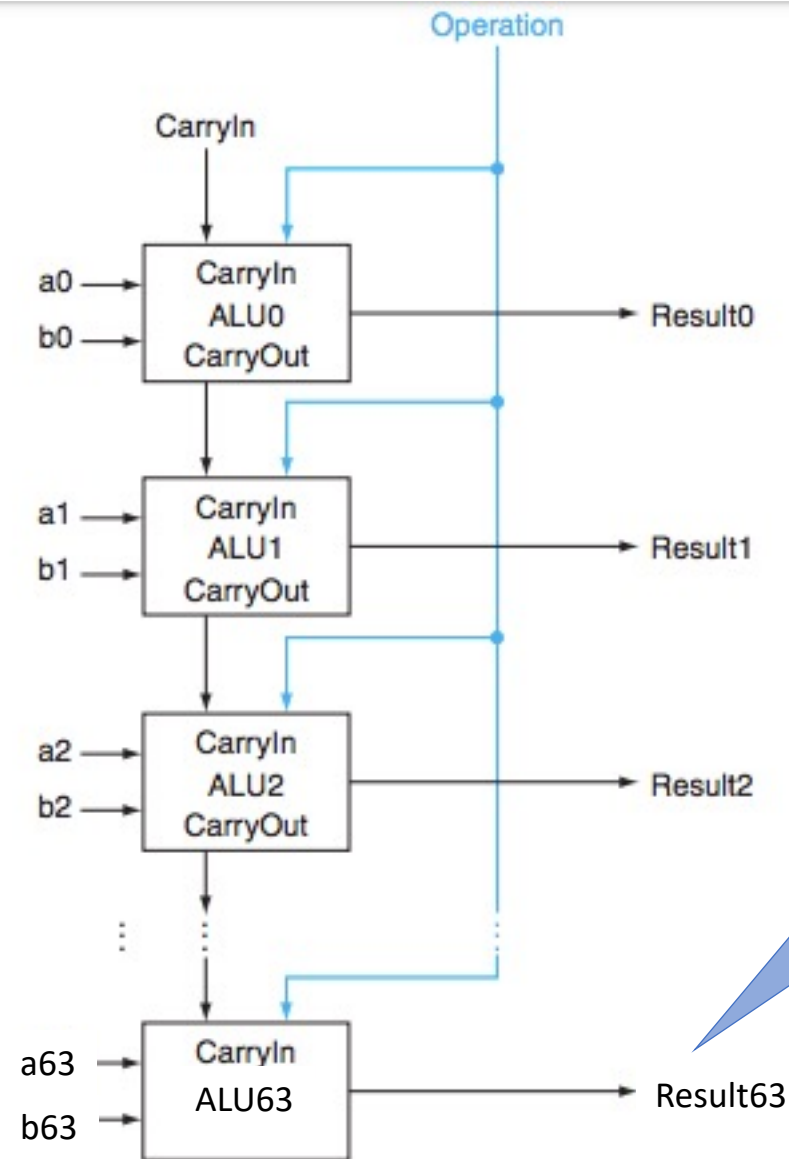


Must wait for sequential evaluation of all 64 1-bit adders

# In search of a faster adder

- Ripple carry:
  - Delay:  $64 * 1\text{BitAdderGateDelay}$ , Gate count:  $64 * c$
- Brute-force (truth table->PLA)
  - Delay: 2, Gate count:  $O(2^{64+64})$
- Clever designs in between?
- Idea #1: (Carry lookahead) compute multiple carry-bits at a time
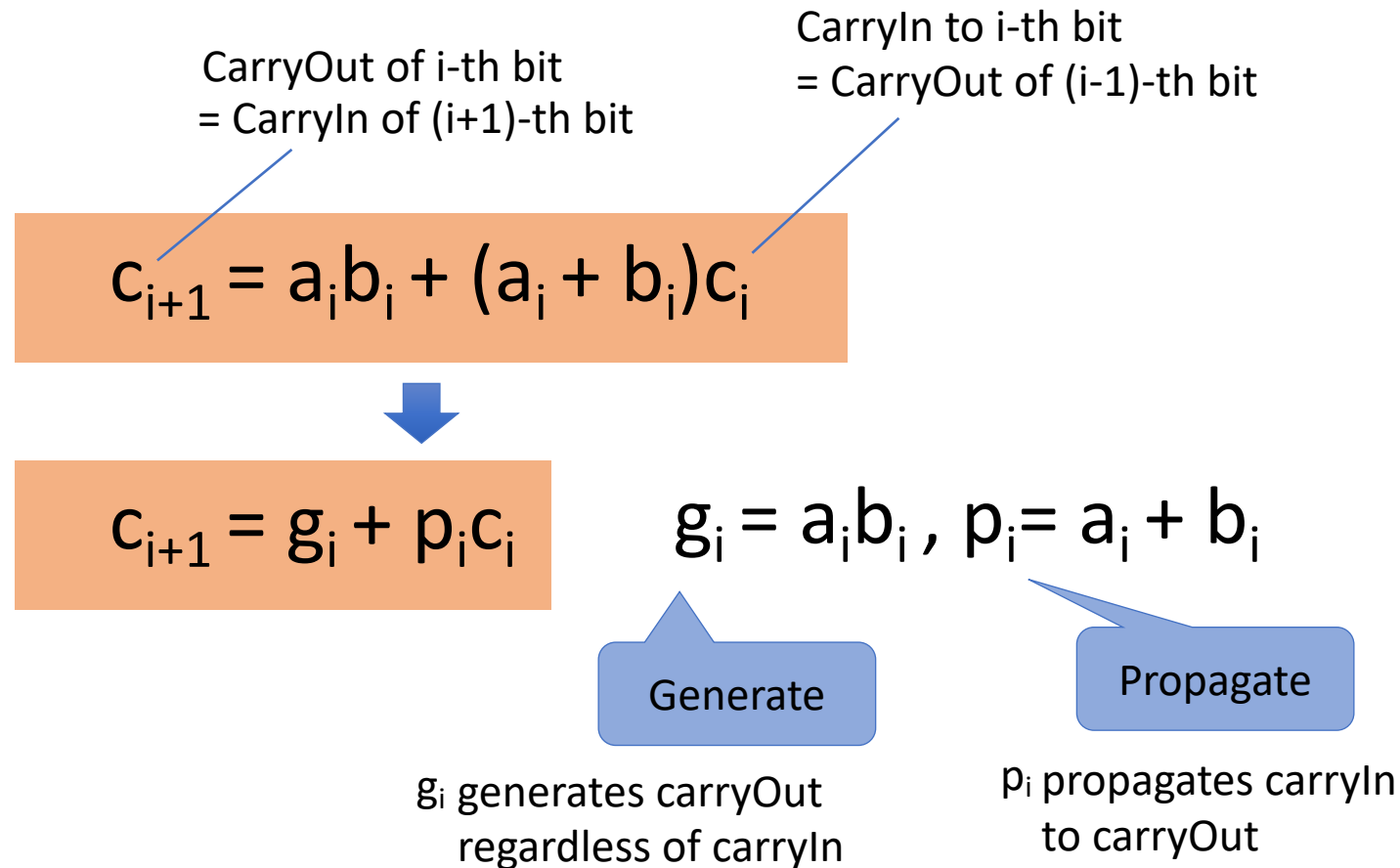
# Faster adder: carry lookahead

- Idea #1: (Carry lookahead) compute multiple carry-bits at a time



# Faster adder: carry lookahead

- Idea #1: (Carry lookahead) compute multiple carry-bits at a time

Computing all carry-bits of a 4-bit adder:

$$c1 = g0 + (p0 \cdot c0)$$

$$c2 = g1 + (p1 \cdot g0) + (p1 \cdot p0 \cdot c0)$$

$$c3 = g2 + (p2 \cdot g1) + (p2 \cdot p1 \cdot g0) + (p2 \cdot p1 \cdot p0 \cdot c0)$$

$$c4 = g3 + (p3 \cdot g2) + (p3 \cdot p2 \cdot g1) + (p3 \cdot p2 \cdot p1 \cdot g0) \\ + (p3 \cdot p2 \cdot p1 \cdot p0 \cdot c0)$$

Delay? 3      4-bit ripple carry  
delay: 2 \* 4

# Faster adder: carry lookahead

- Idea #1: (Carry lookahead) compute multiple carry-bits at a time


Computing all result bits in a 4-bit adder:

$$s_i = \bar{c}_i \cdot a_i \cdot b_i + c_i \cdot \bar{a}_i \cdot b_i + c_i \cdot a_i \cdot \bar{b}_i, \quad i = 0, \dots, 3$$


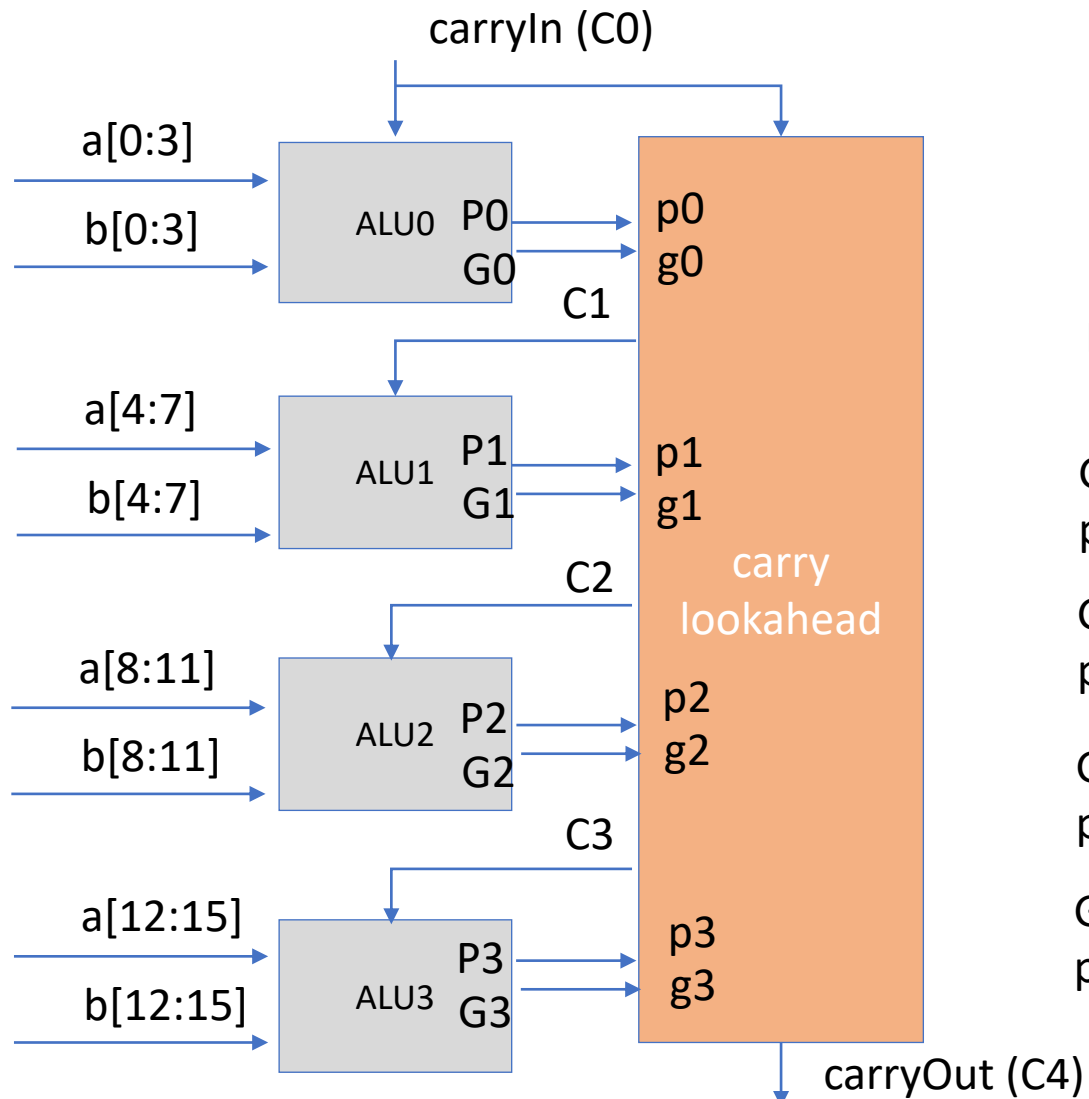
# Faster adder: carry lookahead

- Build a 16-bit adder with carry-ahead 4-bit adders



$$P0 = p3 \cdot p2 \cdot p1 \cdot p0$$

$$P1 = p7 \cdot p6 \cdot p5 \cdot p4$$

$$P2 = p11 \cdot p10 \cdot p9 \cdot p8$$

$$P3 = p15 \cdot p14 \cdot p13 \cdot p12$$

$$C1 = G0 + P0 \cdot C0$$

$$C2 = G1 + P1 \cdot G0 + P1 \cdot P0 \cdot C0$$

$$C3 = G2 + P2 \cdot G1 + P2 \cdot P1 \cdot G0 + P2 \cdot P1 \cdot P0 \cdot C0$$

$$C4 = G3 + P3 \cdot G2 + P3 \cdot P2 \cdot G1 + P3 \cdot P2 \cdot P1 \cdot G0 + P3 \cdot P2 \cdot P1 \cdot P0 \cdot C0$$

$$G0 = g3 + p3 \cdot g2 + p3 \cdot p2 \cdot g1 + p3 \cdot p2 \cdot p1 \cdot g0$$

$$G1 = g7 + p7 \cdot g6 + p7 \cdot p6 \cdot g5 + p7 \cdot p6 \cdot p5 \cdot g4$$

$$G2 = g11 + p11 \cdot g10 + p11 \cdot p10 \cdot g9 + p11 \cdot p10 \cdot p9 \cdot g8$$

$$G3 = g15 + p15 \cdot g14 + p15 \cdot p14 \cdot g13 + p15 \cdot p14 \cdot p13 \cdot g12$$


# Two types of logic circuits

- Combinatorial circuit
  - Truth table  $\rightarrow$  sum of products
  - ROM
- Sequential circuit
  - output is dependent on both input and state (memory elements)

Today's lesson




# Sequential logic requires clock

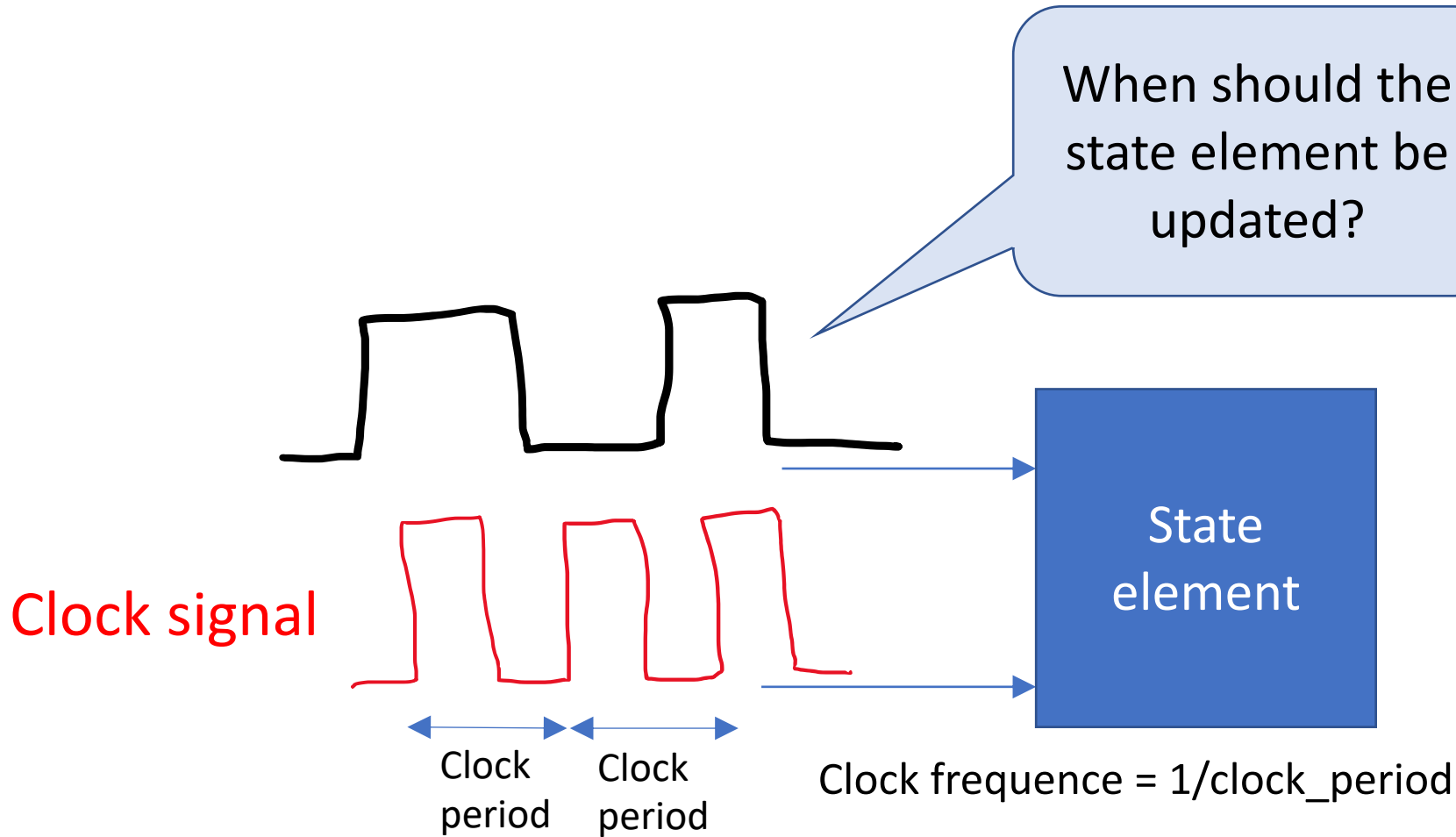

 
# Clocks


- Edge-triggered clocking: state content only changes on active clock edge




# Sequential logic requires clock

 

# Sequential logic requires clock

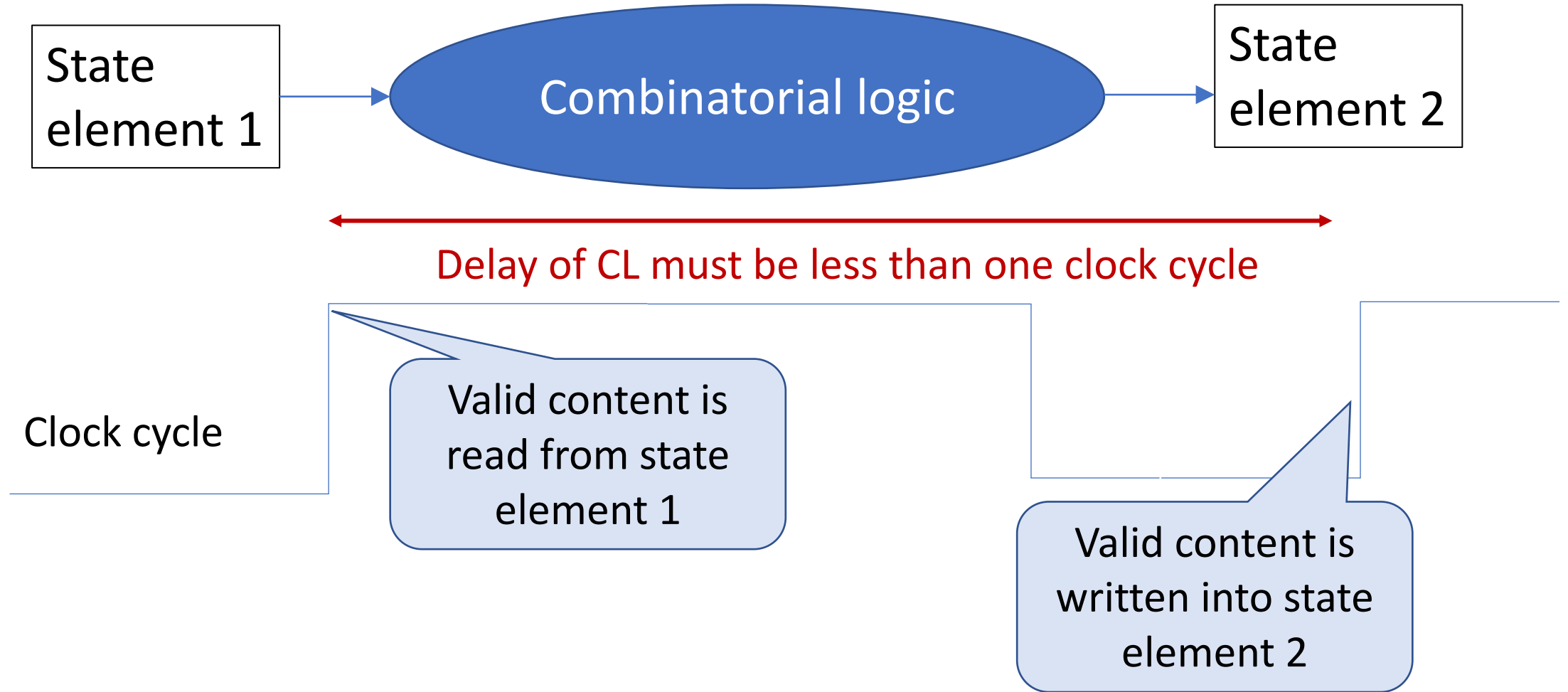


# Sequential logic requires clock

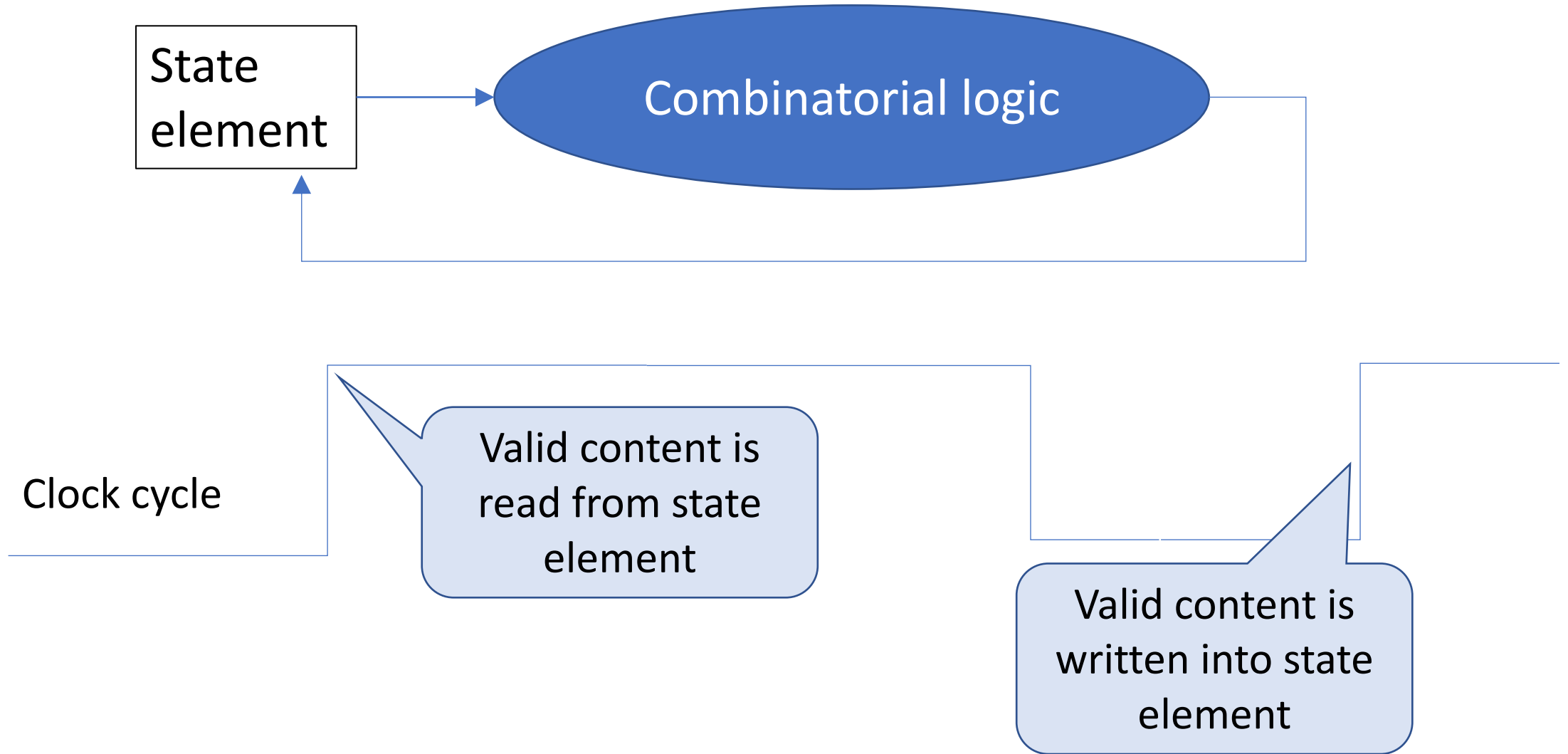

# Memory (state) elements: unlocked S-R Latch


S (set)	R (reset)	
0	0	
1	0	
0	1	
1	1	

 




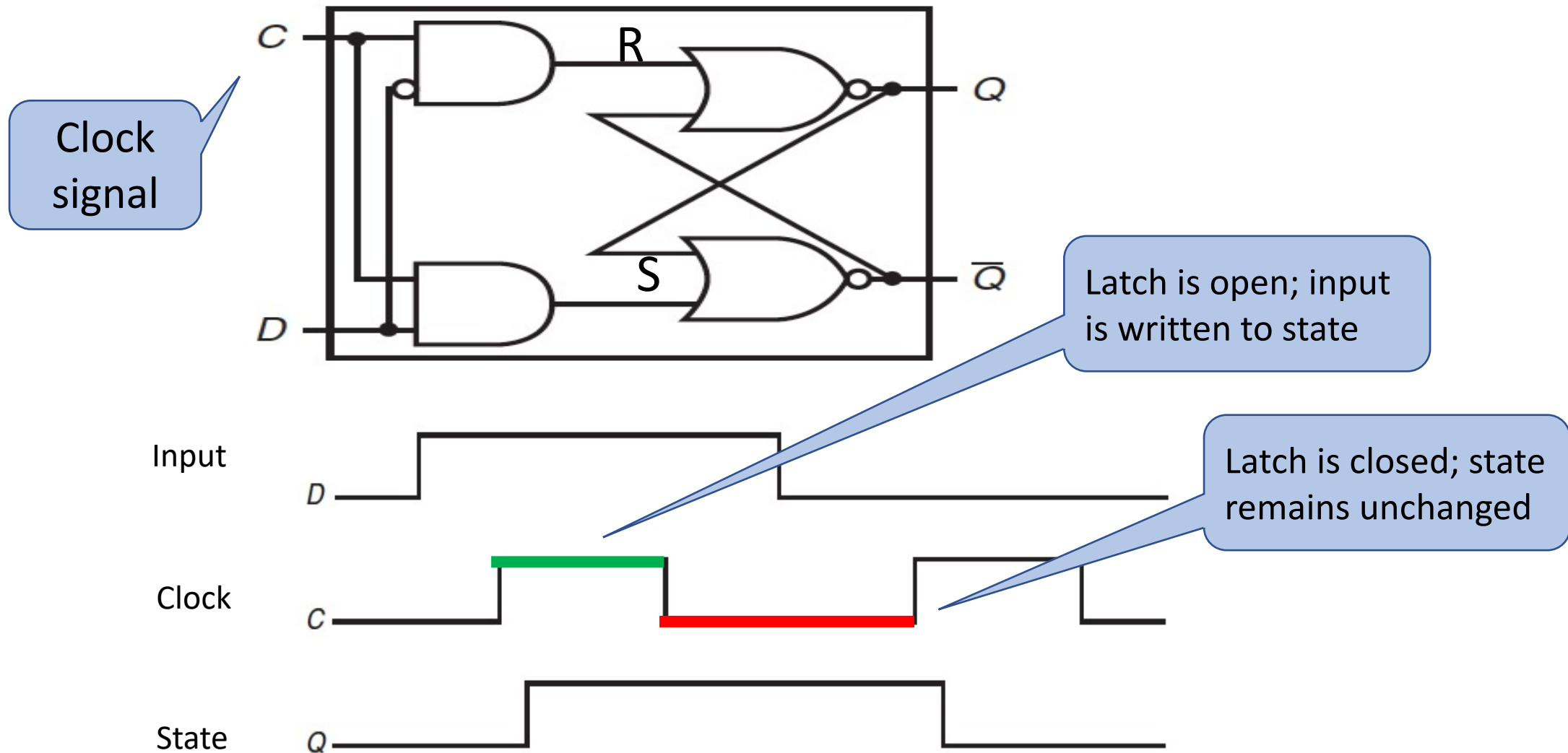
# Memory element: clocked D latch

- D latch: state is changed as long as clock is asserted


 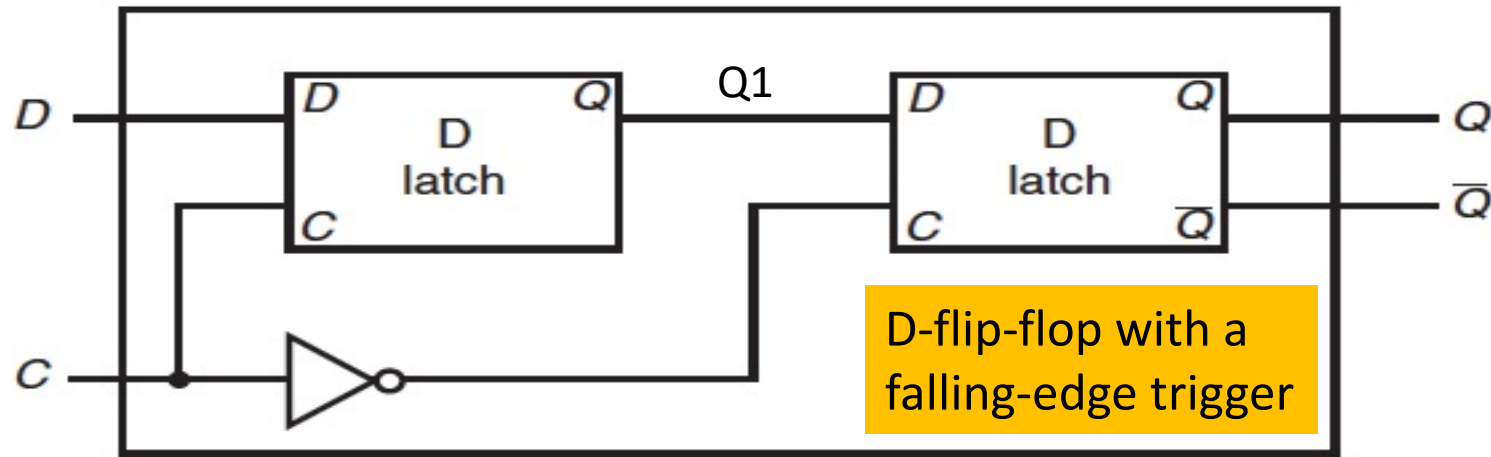
# Memory element: Flip-flop


- Flip-flop: state is changed only on (rising or falling) clock edge




# Finite State Machine

- Combinatorial logic  $\rightarrow$  truth table
- Sequential logic  $\rightarrow$  F(inite) S(tate) M(achine)
  - Input and current state determine next state and outputs

# Finite State Machine

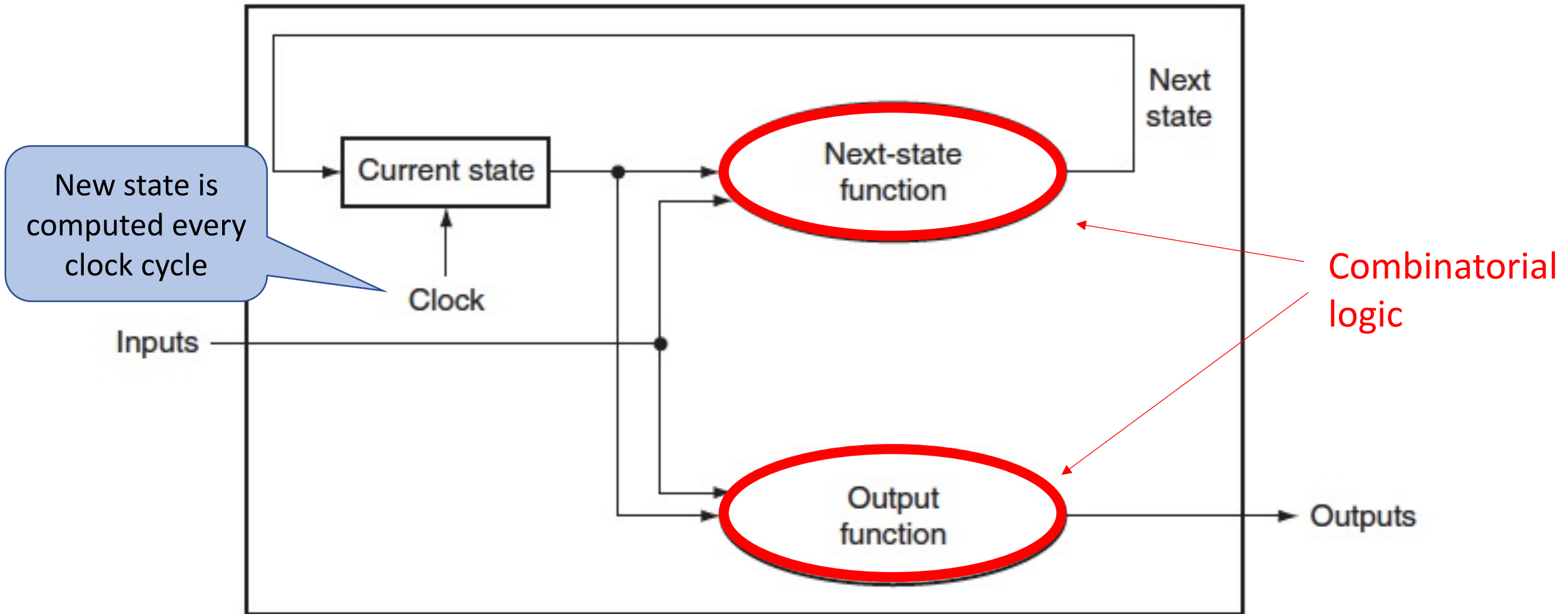

# FSM example: traffic light control

 

State:

NSgreen: traffic light is green in N-S (red in E-W)

EWgreen: traffic light is green in E-W (red in N-S)

Inputs:

NScar: car detected in N-S



EWcar: car detected in E-W

Outputs:

NSlite: 1 if state=NSgreen

EWlite: 1 if state=EWgreen

# FSM example: traffic light control

  


Clock cycles once every 30 seconds

# FSM example: traffic light

- FSM is determined by NextState function and Output function

How many bits  
needed to  
represent state?

	Inputs		
		EWcar	Next state
NSgreen	0	0	NSgreen
NSgreen	0	1	EWgreen
NSgreen	1	0	NSgreen
NSgreen	1	1	EWgreen
EWgreen	0	0	EWgreen
EWgreen	0	1	EWgreen
EWgreen	1	0	NSgreen
EWgreen	1	1	NSgreen

 

# FSM example: traffic light

- FSM is determined by NextState function and Output function


Current State	Inputs		Next state
	NScar	EWcar	
0 (Nsgreen)	0	0	0 (Nsgreen)
0 (Nsgreen)	0	1	1 (Ewgreen)
0 (Nsgreen)	1	0	0 (Nsgreen)
0 (Nsgreen)	1	1	1 (Ewgreen)
1 (Ewgreen)	0	0	1 (Ewgreen)
1 (Ewgreen)	0	1	1 (Ewgreen)
1 (Ewgreen)	1	0	0 (Nsgreen)
1 (Ewgreen)	1	1	0 (Nsgreen)

$$\begin{aligned}
 \text{Next} = & \overline{\text{Curr}} \cdot \overline{\text{NScar}} \cdot \text{EWcar} \\
 & + \overline{\text{Curr}} \cdot \text{NScar} \cdot \text{EWcar} \\
 & + \text{Curr} \cdot \overline{\text{NScar}} \cdot \overline{\text{EWcar}} \\
 & + \text{Curr} \cdot \overline{\text{NScar}} \cdot \text{EWCar}
 \end{aligned}$$


 
# FSM traffic light: next state function

$$Next = \overline{Curr} \cdot EWcar + Curr \cdot \overline{NScar}$$




# FSM traffic light: output function

	Outputs	
	NSlite	EWlite
0 NSgreen	1	0
1 EWgreen	0	1

$$\text{NSLite} = \overline{\text{Curr}}$$


$$\text{EWLite} = \text{Curr}$$

# FSM traffic light: output function

 

# Another FSM example: Electronic eye

State transition diagram?

 


Lights are lit from left to right, then right to left and so on

# Summary

- Memory (state) elements
  - Requires a clock signal to know when to update state value
  - Unclocked S-R latch → Clocked D latch → Flip-flop
- Sequential logic
  - Finite state machine
  - Decompose into two CL functions
    - Next state function: compute next state value based on current state value and inputs
    - Output function: compute output based on current state value and inputs


# Happy Thanksgiving!

 


## Stay safe!
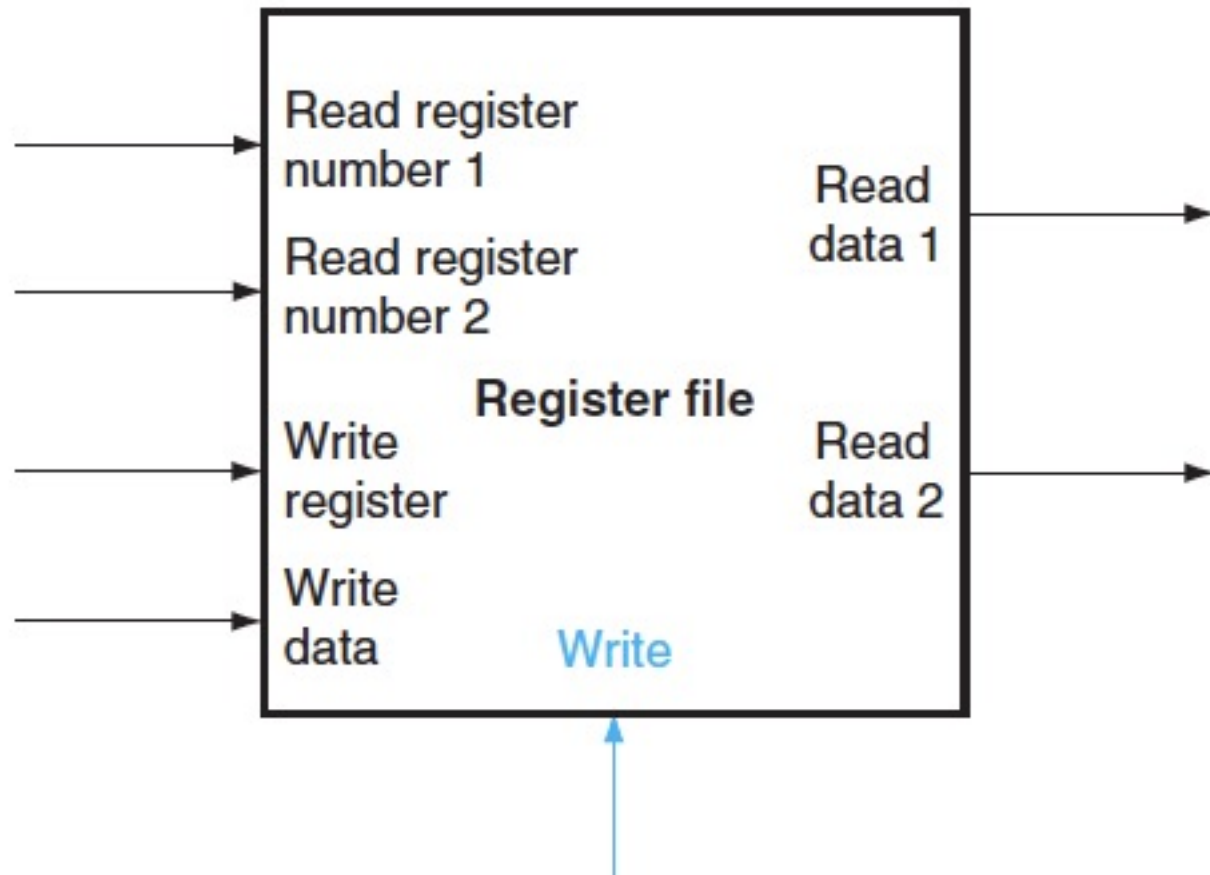
# Memory element: Register file

- Register file: a set of registers that can be read and written




😞 Why reading two registers at a time?

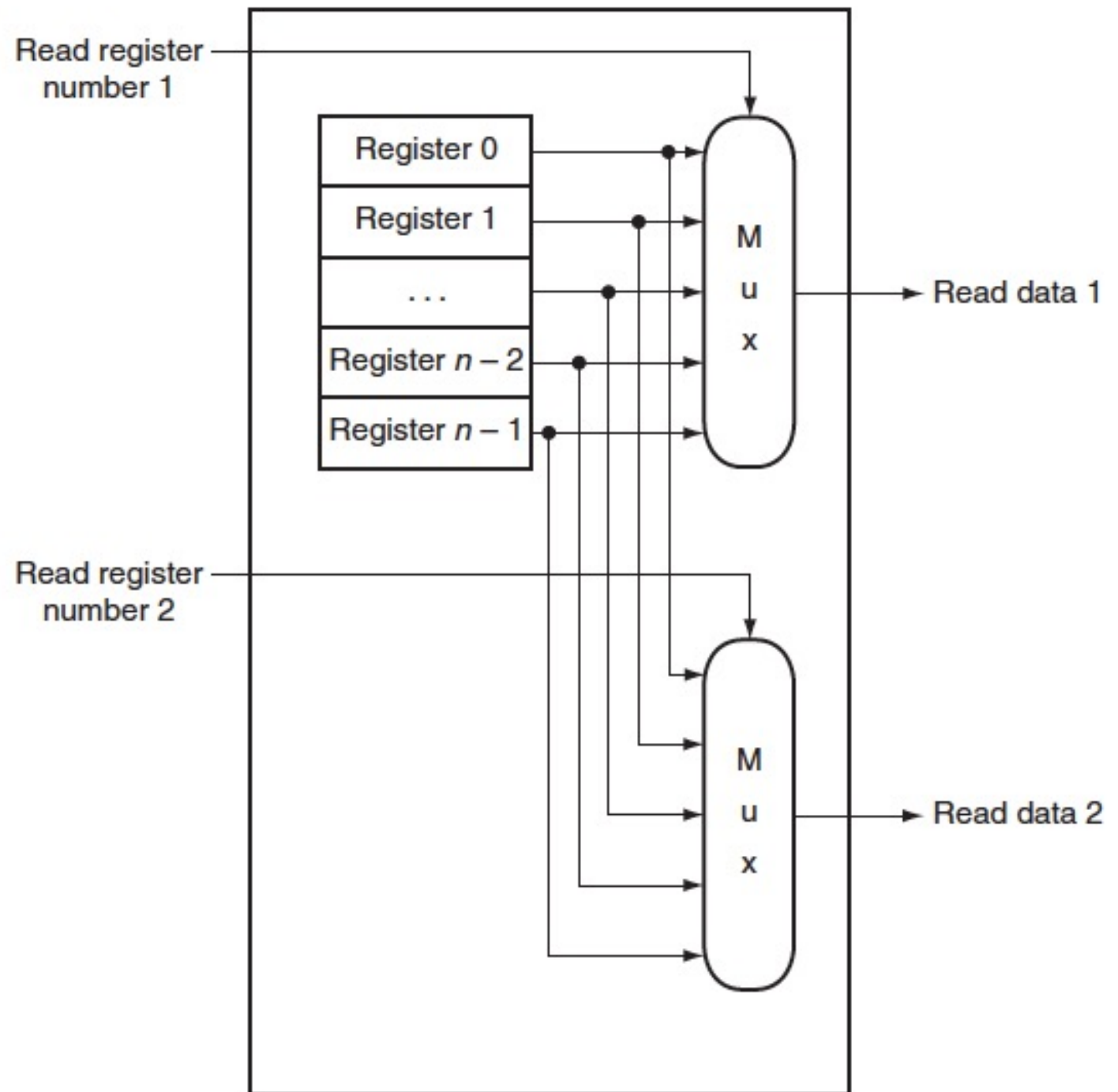

Clock signal is assumed and not drawn



Register file:  
Write

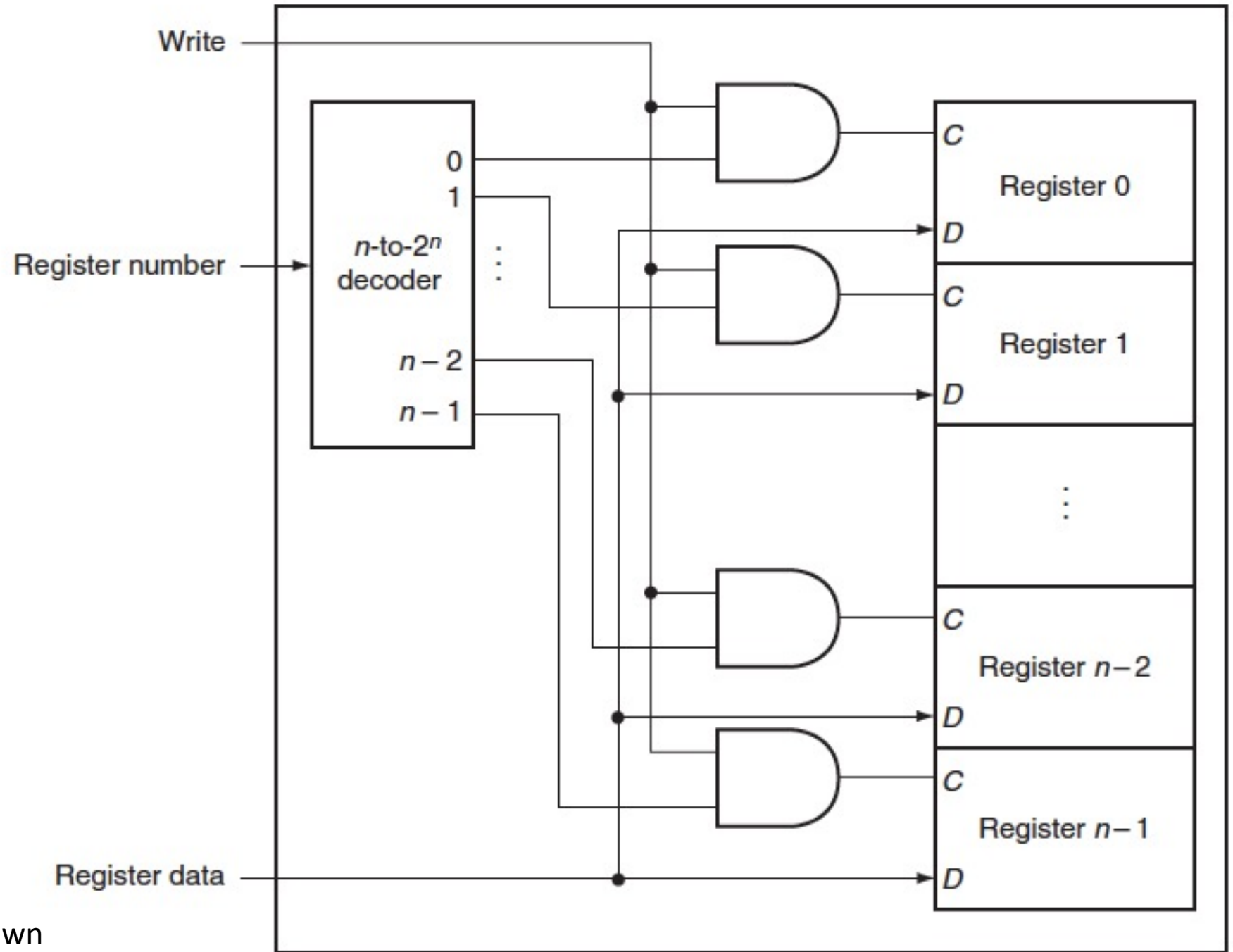

Clock signal is assumed and not drawn

# Register file

- What if the same register is read and written in the same clock cycle?
  - Return register value written in an earlier cycle
  - Write of new value occurs on the clock edge (at the end of the current cycle)
- Some register file can read value currently being written
  - Requires additional logic in the register file