

# Sequential Logic

Jinyang Li


# What we've learnt so far

- Combinatorial logic
  - Truth table  $\rightarrow$  sum of products circuits
  - E.g. Multiplexors (Mux), Decoders
- ALU
  - Ripple carry
  - Carry lookahead

# Two types of logic circuits


- Combinatorial circuit
  - Truth table  $\rightarrow$  sum of products
  - ROM
- Sequential circuit
  - output is dependent on both input and state (memory elements)

Today's lesson

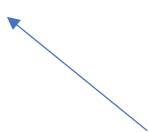

# ROM-based implementation of CL

- ROM (read-only memory)

 

ROM of 2 address lines and 5 bits per entry

# ROM-based implementation of CL

Example CL : Count # of 1's in 3-bit inputs

A	B	C	out <sub>1</sub>	out <sub>0</sub>
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	1
1	1	0	1	1
1	1	1	0	0




000:	00
001:	01
010:	01
011:	10
100:	01
101:	10
110:	10
111:	11

ROM of height 8 width 2
 
# ROM vs. PLA (sum of products)

- ROM contains more entries than PLA ( $2^n$ )



7 products (AND)

More efficient!

000:	00
001:	01
010:	01
011:	10
100:	01
101:	10
110:	10
111:	11


8 entries

Easy!

# Two types of logic circuits

- Combinatorial circuit
  - Truth table  $\rightarrow$  sum of products
  - ROM
- Sequential circuit
  - output is dependent on both input and state (memory elements)


# Sequential logic require clocks

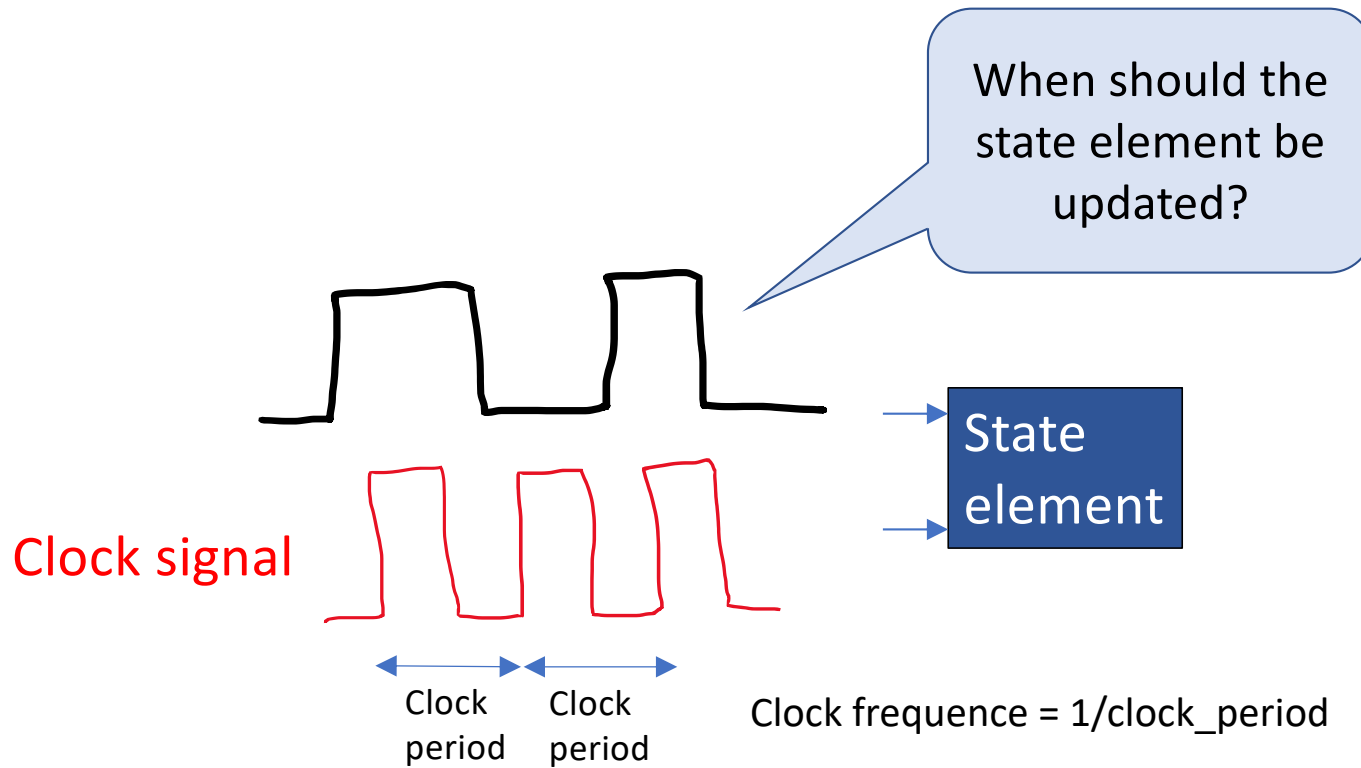



 
# Clocks


- Edge-triggered clocking: state content only changes on active clock edge




# Sequential logic require clocks

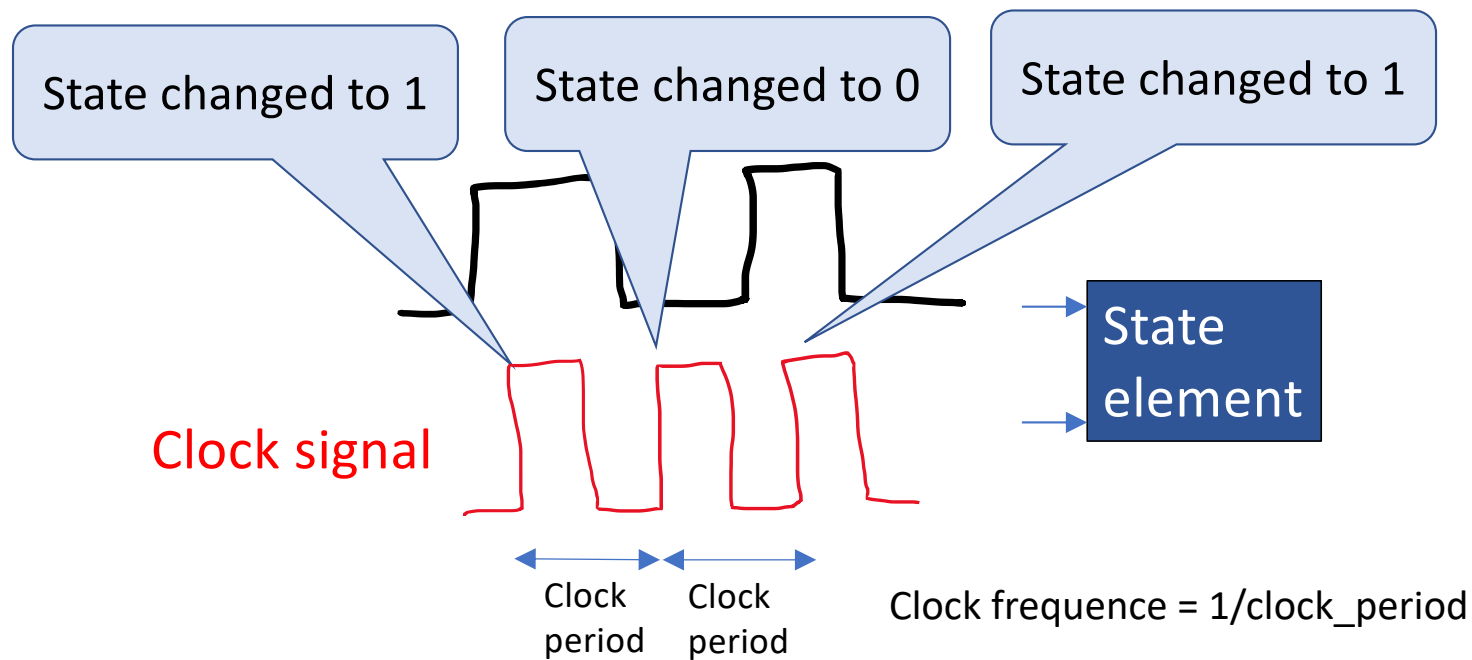

# Sequential logic require clocks

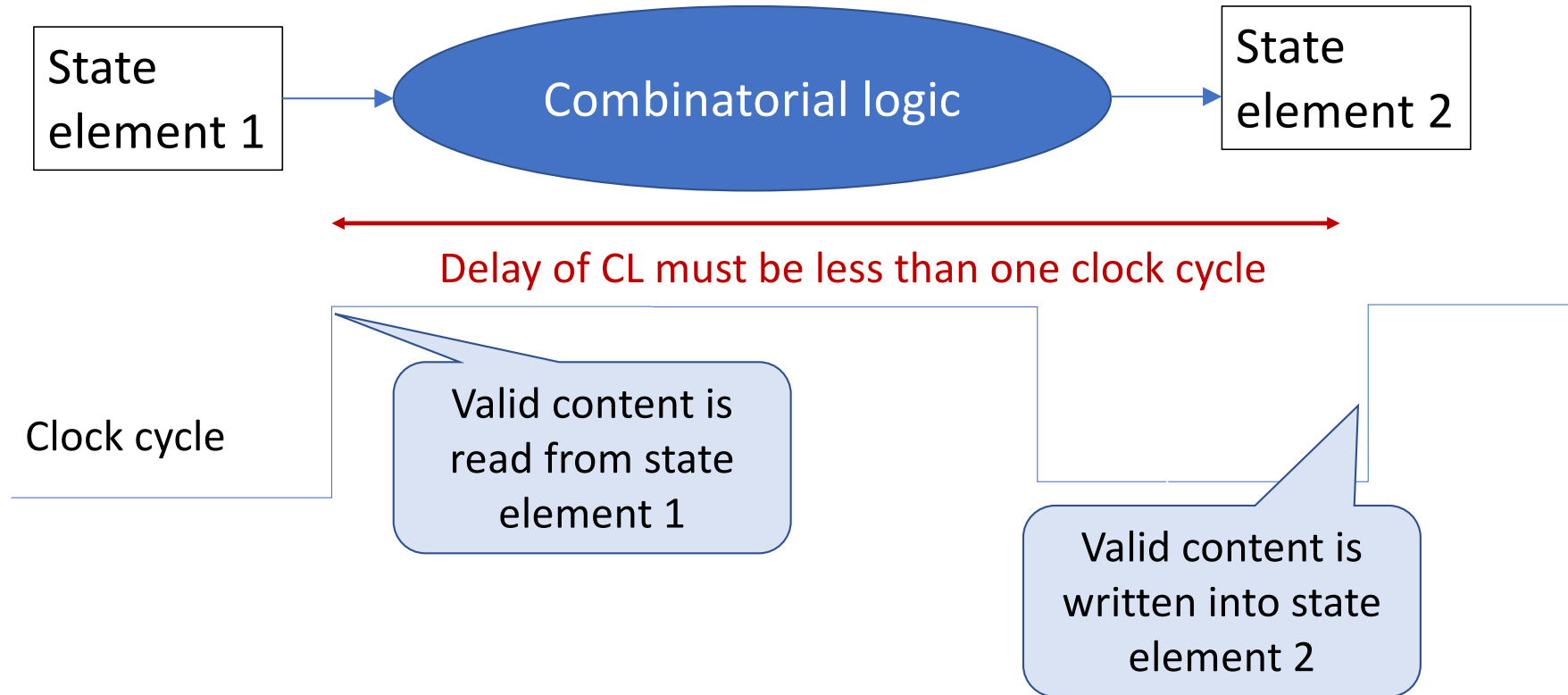


# Sequential logic require clocks

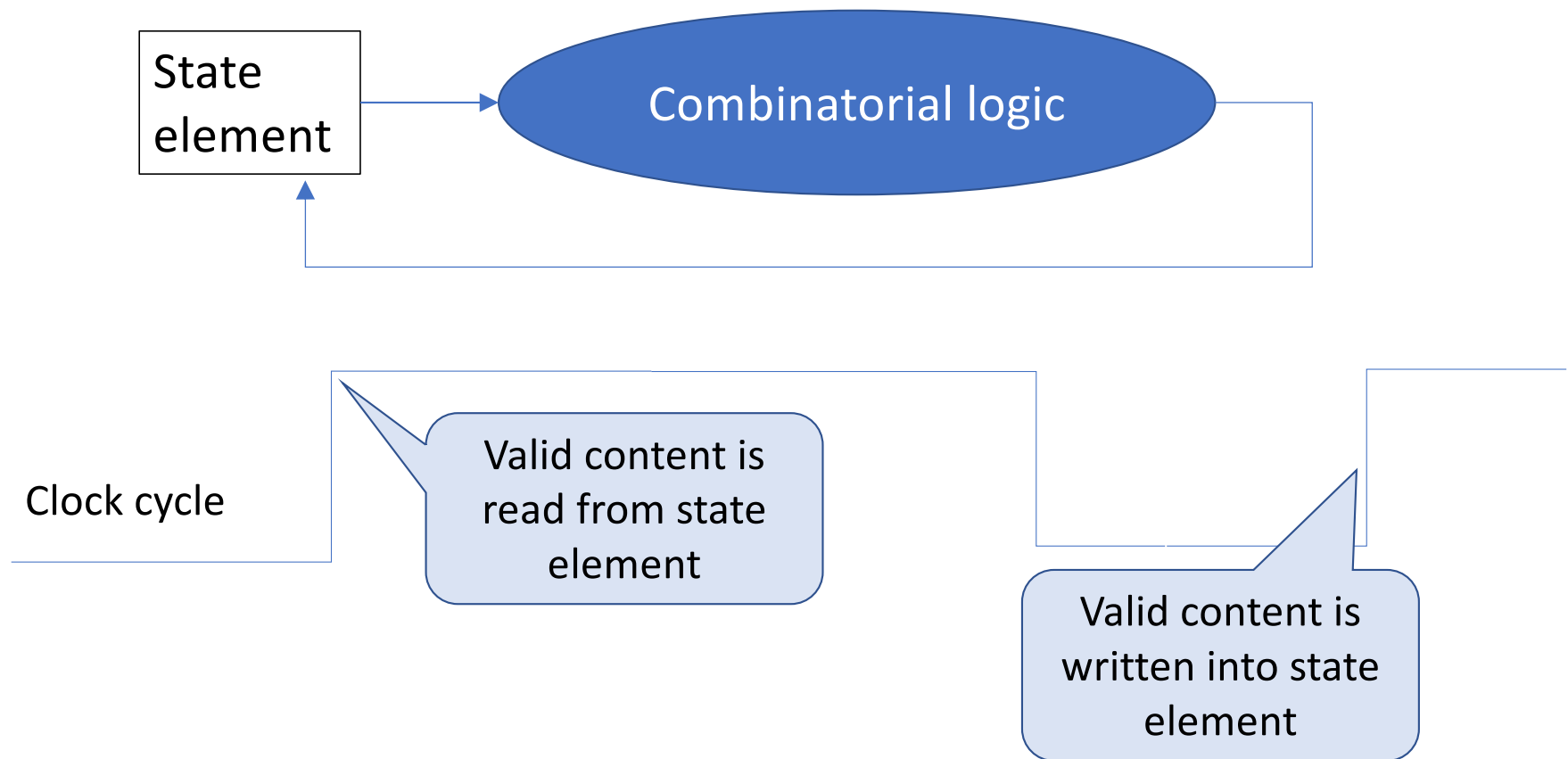


# Memory (state) elements: unlocked S-R Latch

S (set)	R (reset)	
0	0	keeps existing value
1	0	Q=1
0	1	Q=0
1	1	Invalid

 

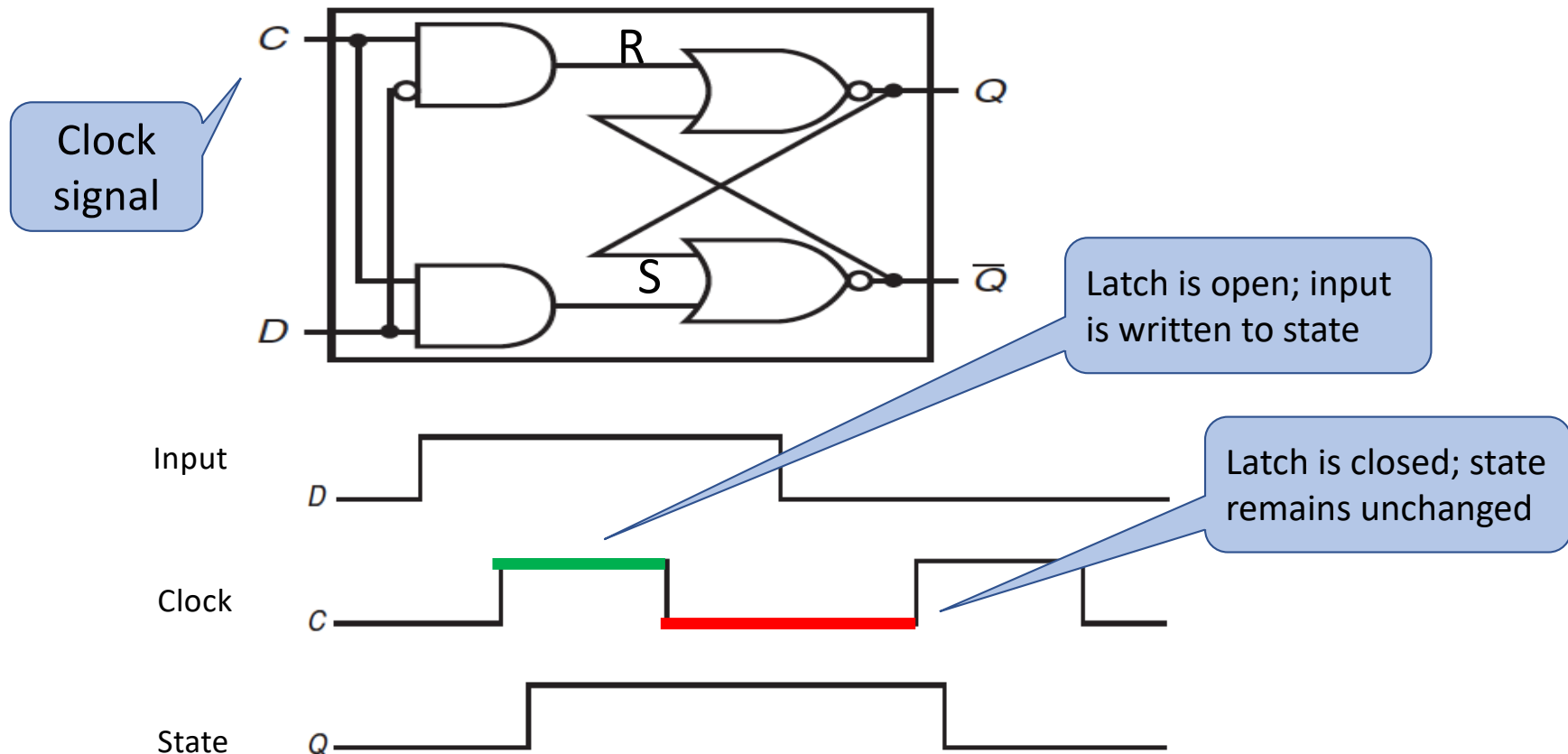
# Memory element: clocked D latch

- D latch: state is changed as long as clock is asserted



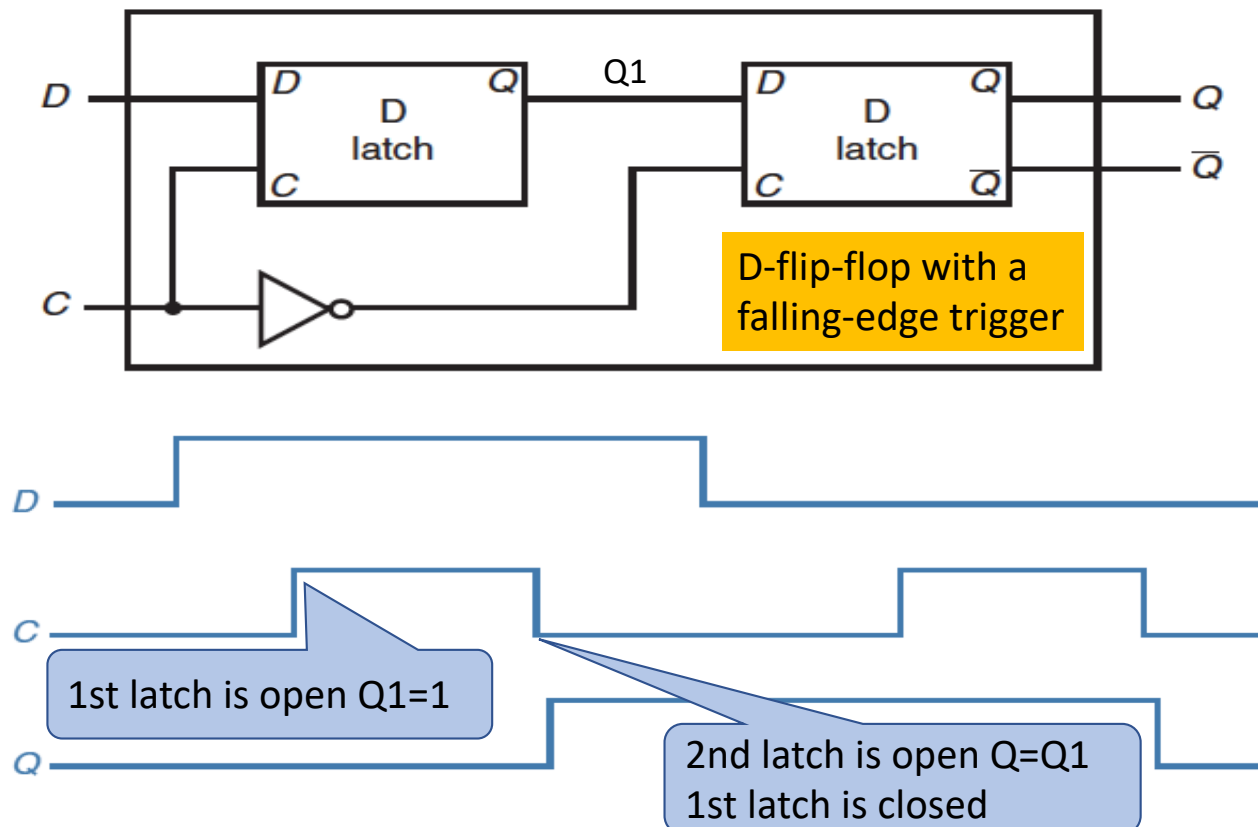
# Memory element: Flip-flop

- Flip-flop: state is changed only on (rising or falling) clock edge




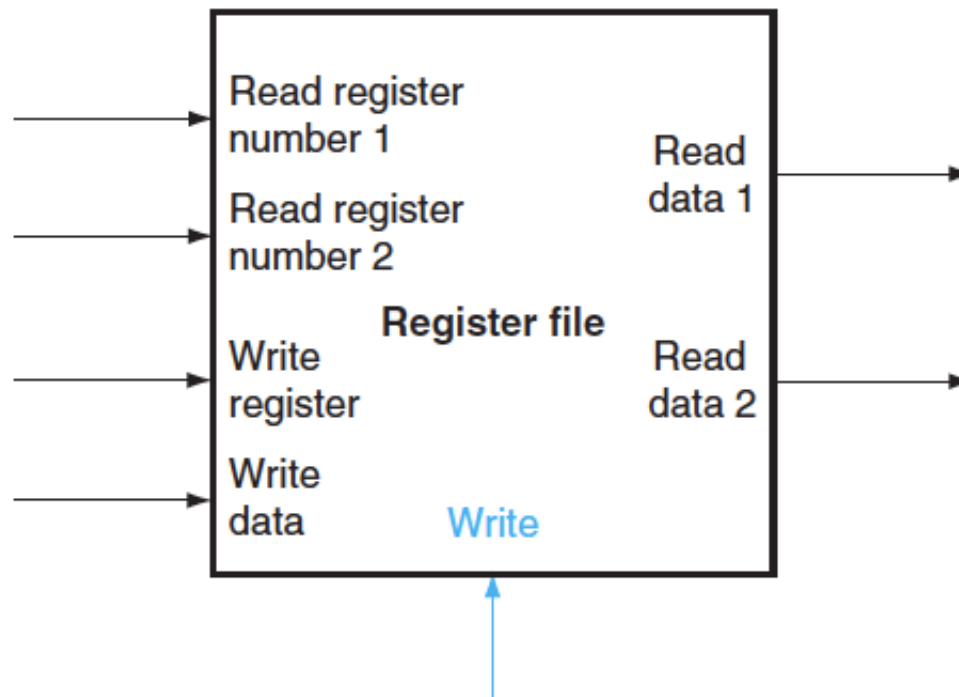
# Memory element: Register file

- Register file: a set of registers that can be read and written





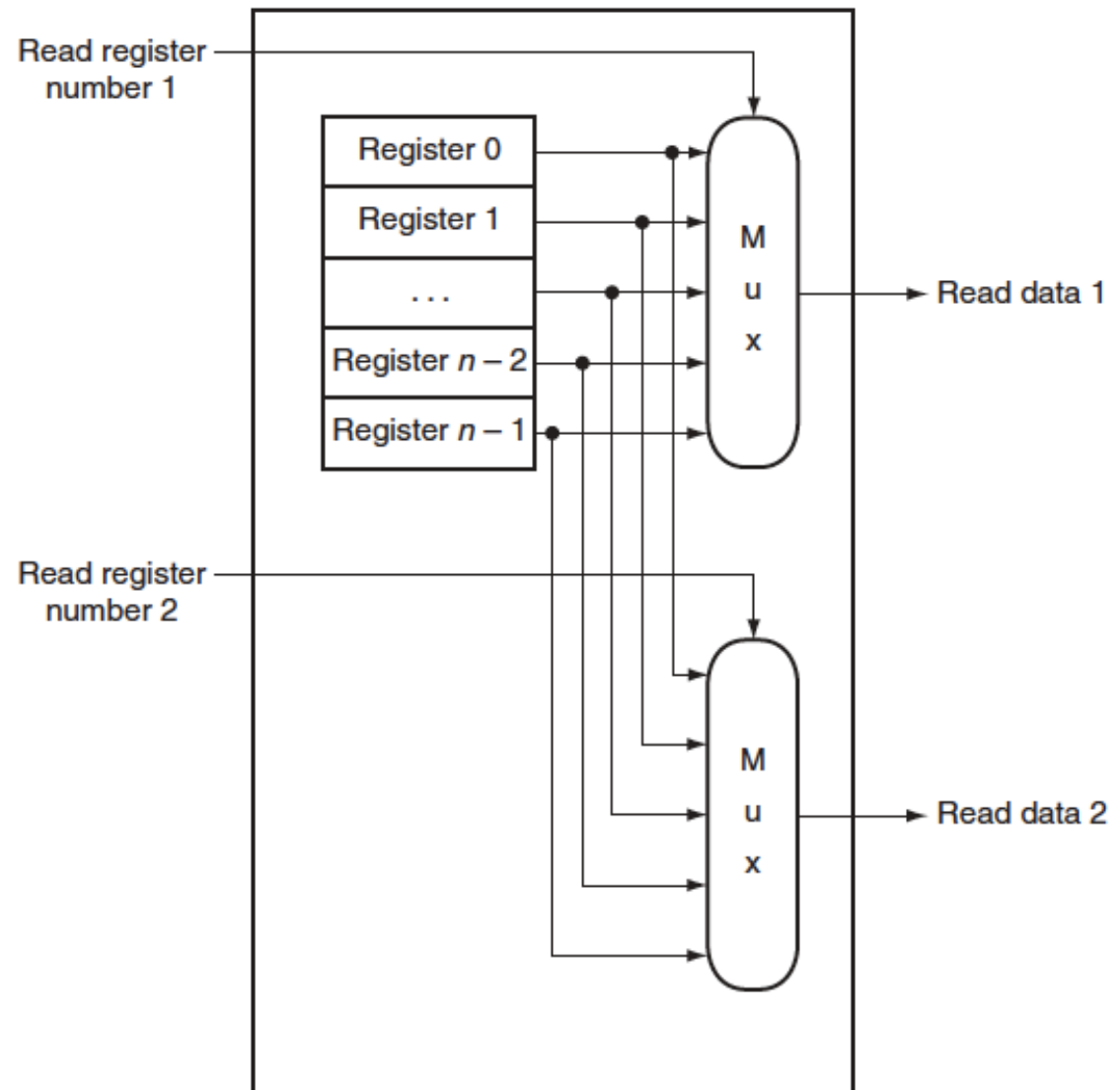

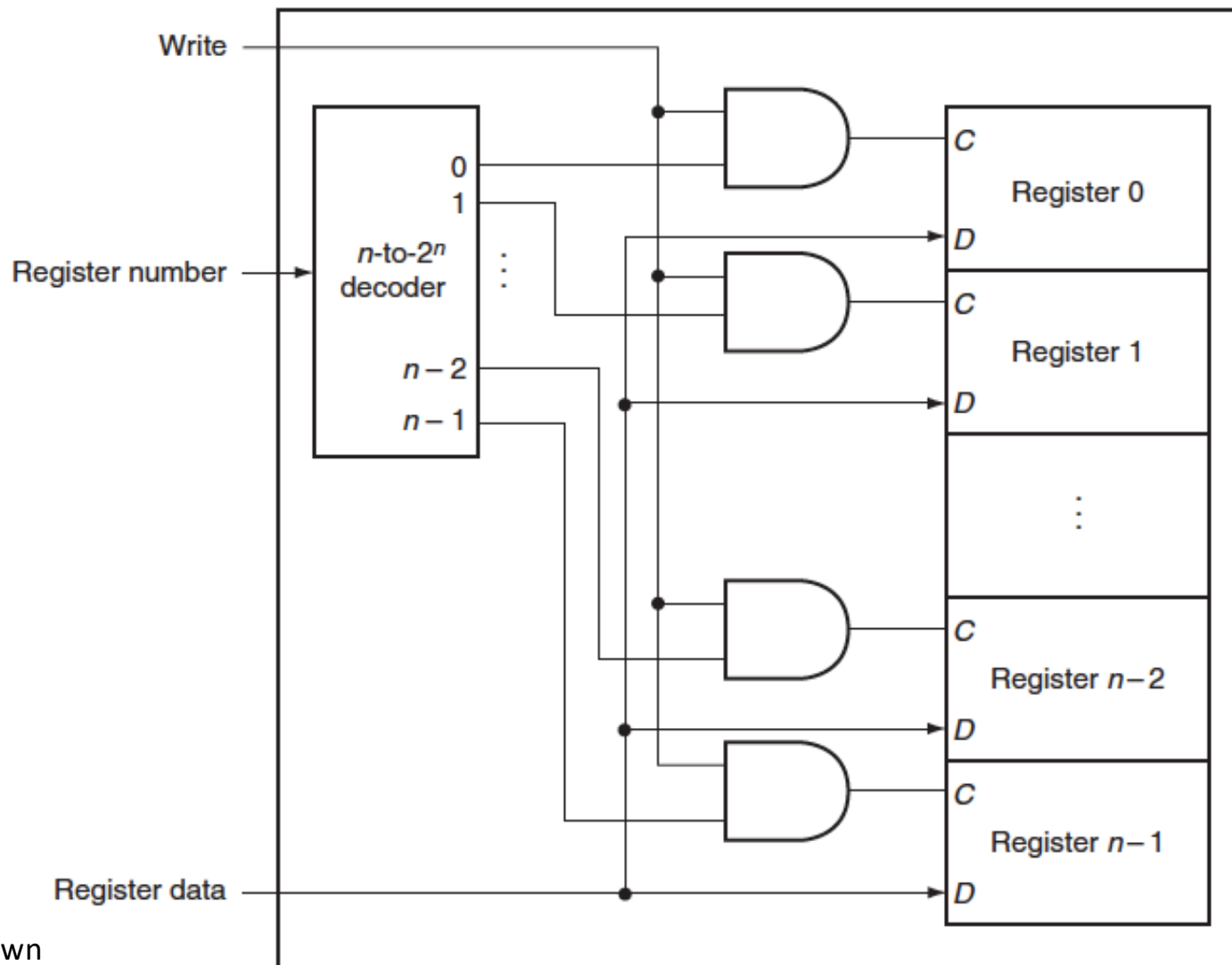

Clock signal is assumed and not drawn


# Register file

- What if the same register is read and written in the same clock cycle?
  - Return value written in an earlier cycle
  - Write of new value occurs on the clock edge (at the end of the current cycle)
- Some register file can read value currently being written
  - Requires additional logic in the register file


# Finite State Machine

- Combinatorial logic  $\rightarrow$  truth table
- Sequential logic  $\rightarrow$  F(inite) S(tate) M(achine)
  - Input and current state determine next state and outputs

# Finite State Machine

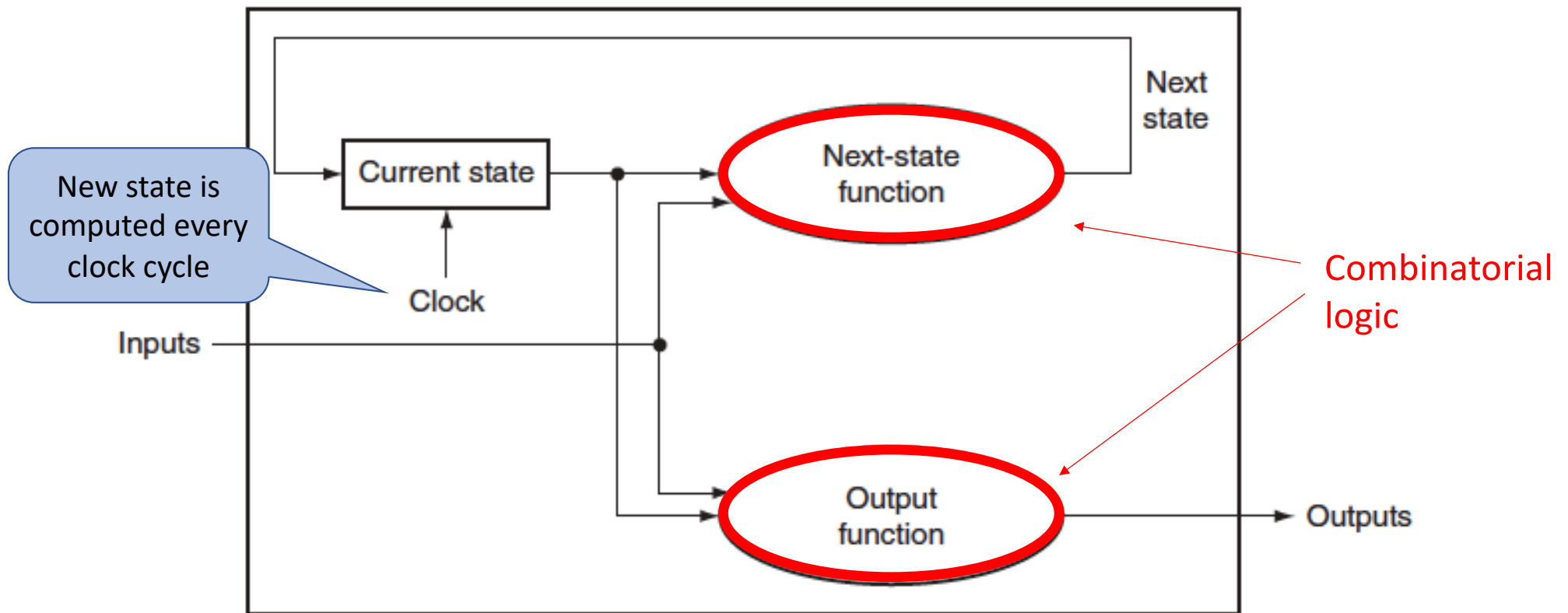

# FSM example: traffic light control

 

State:

NSgreen: traffic light is green in N-S (red in E-W)

EWgreen: traffic light is green in E-W (red in N-S)

Inputs:

NScar: car detected in N-S



EWcar: car detected in E-W

Outputs:

NSlite: 1 if state=NSgreen

EWlite: 1 if state=EWgreen

# FSM example: traffic light control

  


Clock cycles once every 30 seconds

# FSM example: traffic light

- FSM is determined by NextState function and Output function

How many bits  
needed to  
represent state?

	Inputs		
		EWcar	Next state
NSgreen	0	0	NSgreen
NSgreen	0	1	EWgreen
NSgreen	1	0	NSgreen
NSgreen	1	1	EWgreen
EWgreen	0	0	EWgreen
EWgreen	0	1	EWgreen
EWgreen	1	0	NSgreen
EWgreen	1	1	NSgreen

 




# FSM example: traffic light

- FSM is determined by NextState function and Output function

Current State	Inputs		Next state
	NScar	EWcar	
0 (Nsgreen)	0	0	0 (Nsgreen)
0 (Nsgreen)	0	1	1 (Ewgreen)
0 (Nsgreen)	1	0	0 (Nsgreen)
0 (Nsgreen)	1	1	1 (Ewgreen)
1 (Ewgreen)	0	0	1 (Ewgreen)
1 (Ewgreen)	0	1	1 (Ewgreen)
1 (Ewgreen)	1	0	0 (Nsgreen)
1 (Ewgreen)	1	1	0 (Nsgreen)

$$\begin{aligned}
 Next &= \overline{Curr} \cdot \overline{NScar} \cdot EWcar \\
 &\quad + \overline{Curr} \cdot NScar \cdot EWcar \\
 &\quad + Curr \cdot \overline{NScar} \cdot \overline{EWcar} \\
 &\quad + Curr \cdot \overline{NScar} \cdot EWCar \\
 &= \overline{Curr} \cdot EWcar + Curr \cdot \overline{NScar}
 \end{aligned}$$
 
## FSM traffic light: next state function



## FSM traffic light: output function

		Outputs	
		NSlite	EWlite
0	NSgreen	1	0
1	EWgreen	0	1

$$\text{NSLite} = \overline{\text{Curr}}$$

$$\text{EWLite} = \text{Curr}$$

## FSM traffic light: output function

