

Building an ALU

Jinyang

What we've learnt so far


- Basic logic design
 - Logic circuits == Boolean expressions
- How to build a combinatorial logic circuit
 - Specify the truth table
 - Output is the sum of products
- Common CL
 - Decoder
 - Multiplexer

Lesson plan

- 1-bit ALU
- Logical ops: AND/OR/XOR/shift
- Arithmetic ops: addition, subtraction, multiplication, division


Array of logic elements

 - So far, our circuits work on 1-bit inputs/outputs
- How to build circuits with n-bit inputs/outputs?



Array of logic elements

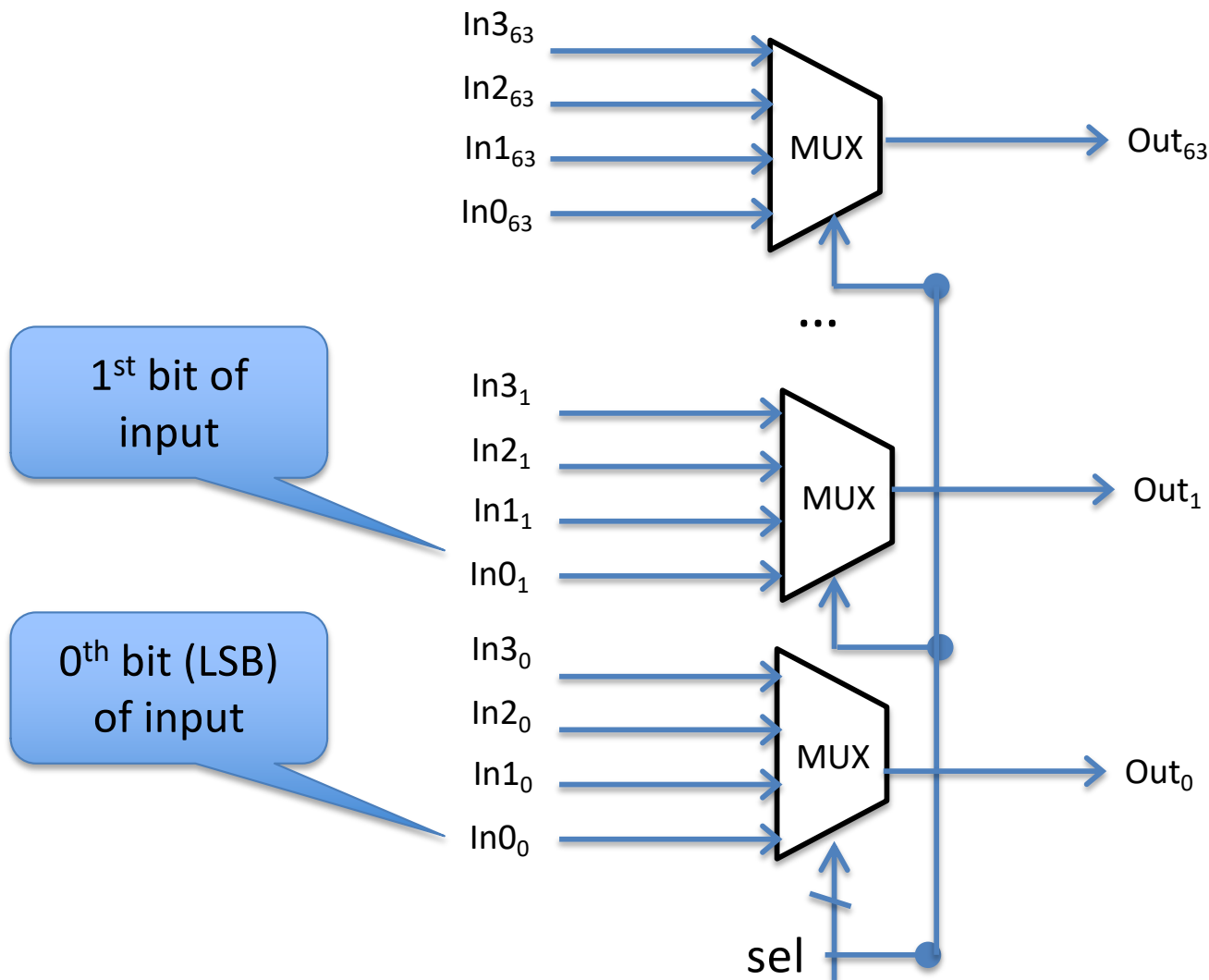- 64-bit multiplexor: an array of 64 1-bit multiplexors



ALU overview


Example

operation


Op	
00	A & B
01	A B
10	A + B




Implementing ALU: AND

 


Implementing ALU: AND

 


Implementing ALU: OR

 


Implementing ALU: adder

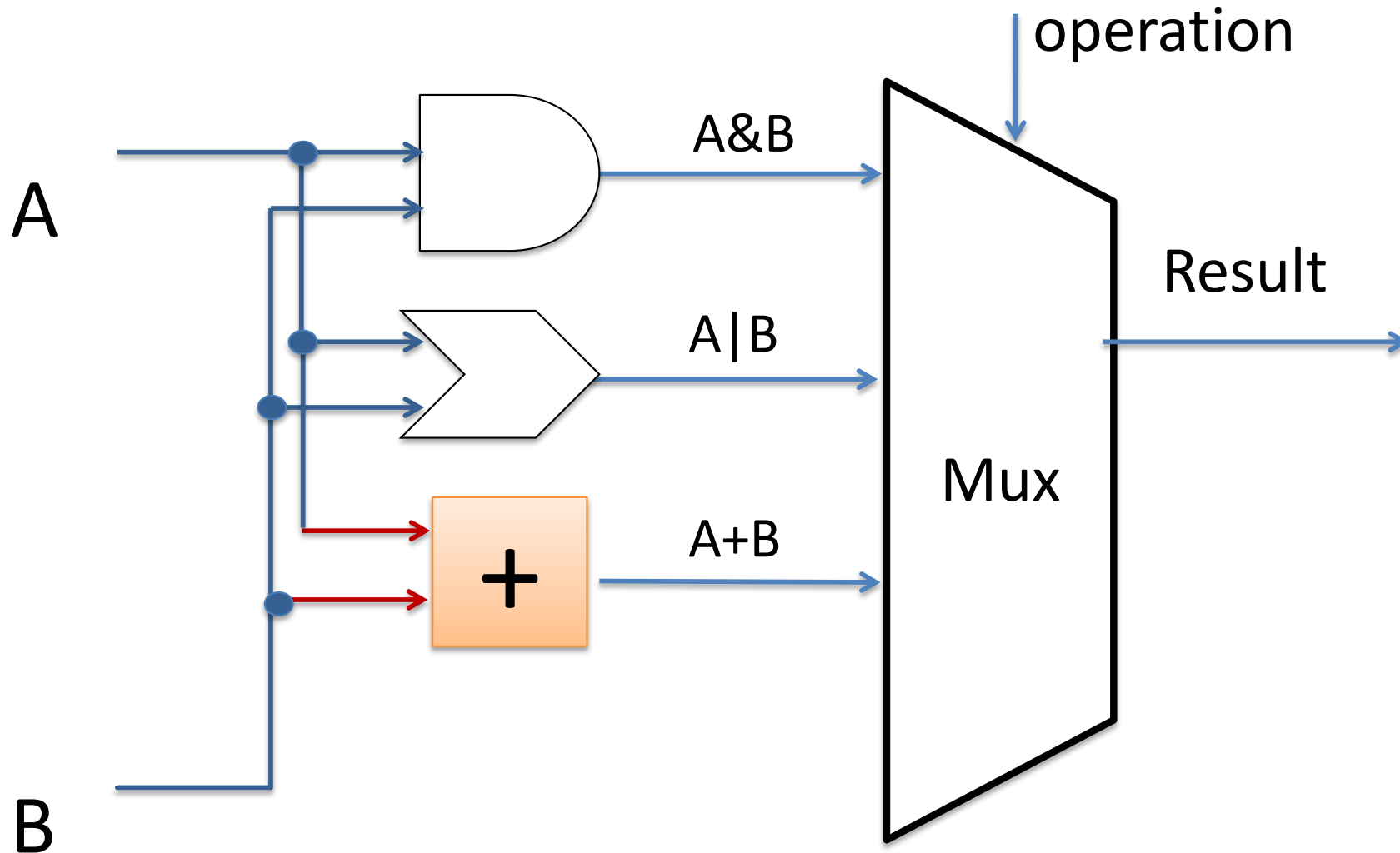

1-bit adder

 

 

1-bit adder


Inputs			Outputs	
a	b	CarryIn	CarryOut	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Brute force PLA

1-bit adder

- We can do better than PLA for CarryOut
 
$$\text{CarryOut} = (b \cdot \text{CarryIn}) + (a \cdot \text{CarryIn}) + (a \cdot b)$$



1-bit adder

$$\text{Sum} = (a \cdot \bar{b} \cdot \overline{\text{CarryIn}}) + (\bar{a} \cdot b \cdot \overline{\text{CarryIn}}) + (\bar{a} \cdot \bar{b} \cdot \text{CarryIn}) + (a \cdot b \cdot \text{CarryIn})$$


Inputs			Outputs	
a	b	CarryIn	CarryOut	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Subtraction


- Idea: $a - b = a + (-b)$
- How to calculate 2's complement?

Subtraction in 1-bit ALU


Set Binvert=1
carryIn=1
Op=(10)₂
to compute A-B

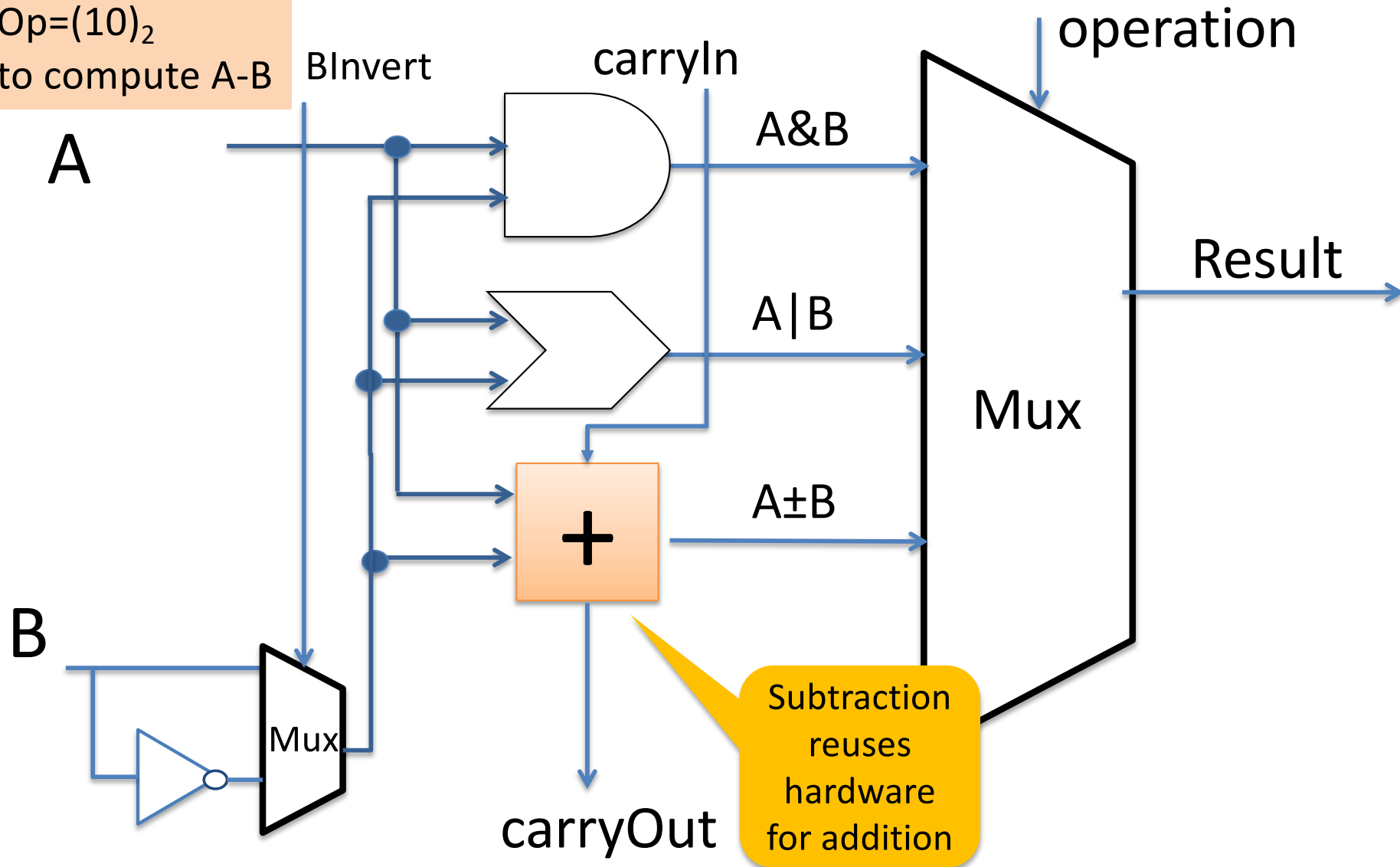

Extend 1-bit ALU to 64-bit

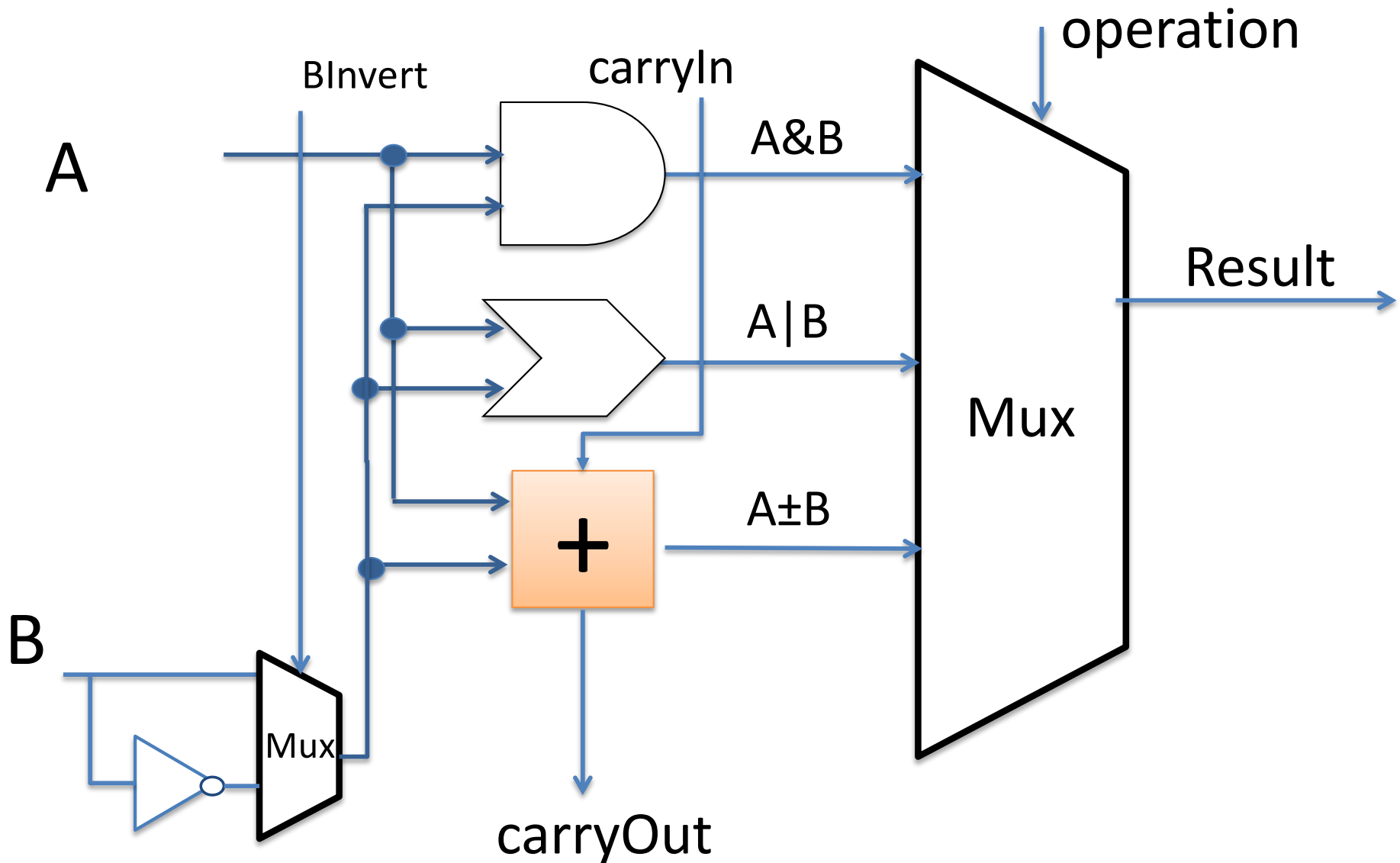


Simple 64-bit adder: ripple carry

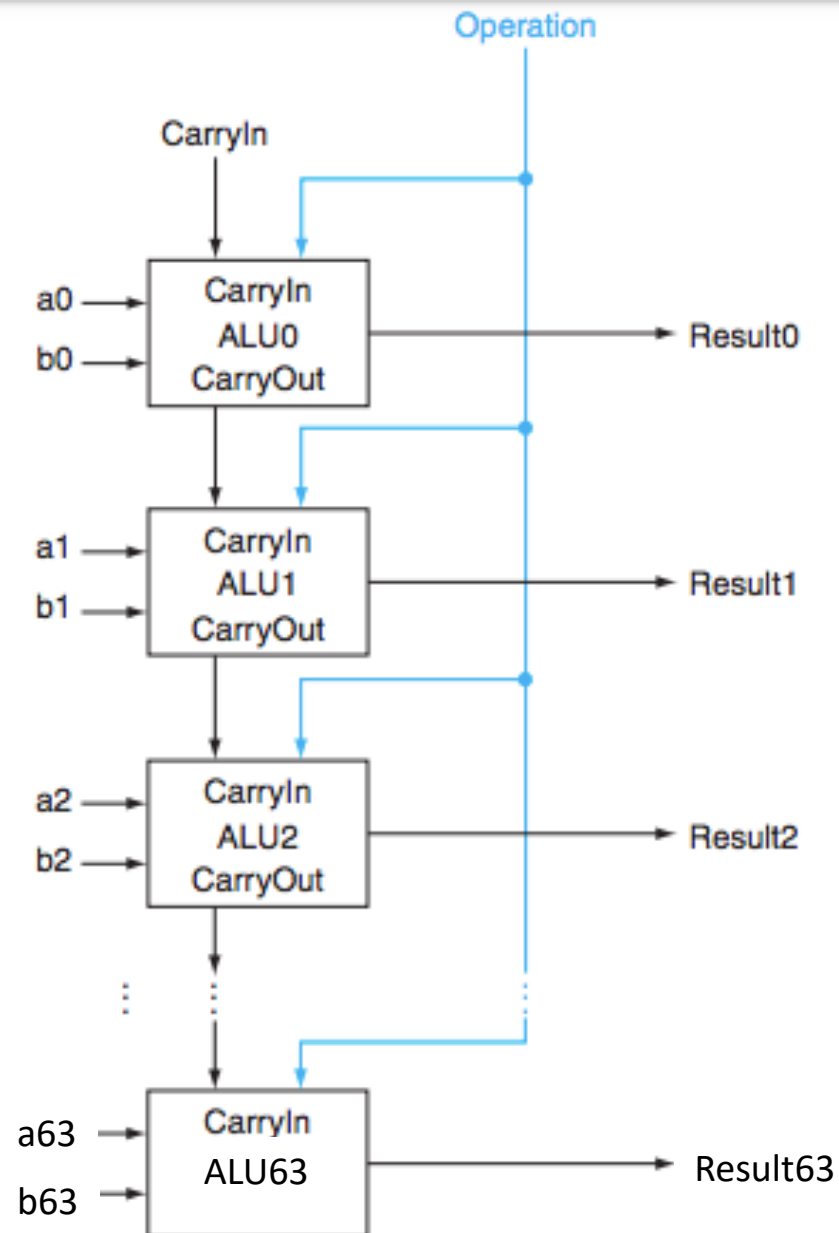


Extend ALU to include slt

 - RISC-V slt instruction: Result = (A < B) ? 1 : 0 Signed
 - X86 equivalent: `cmpq %rbx,%rax setl %rcx`




Extend ALU to include slt

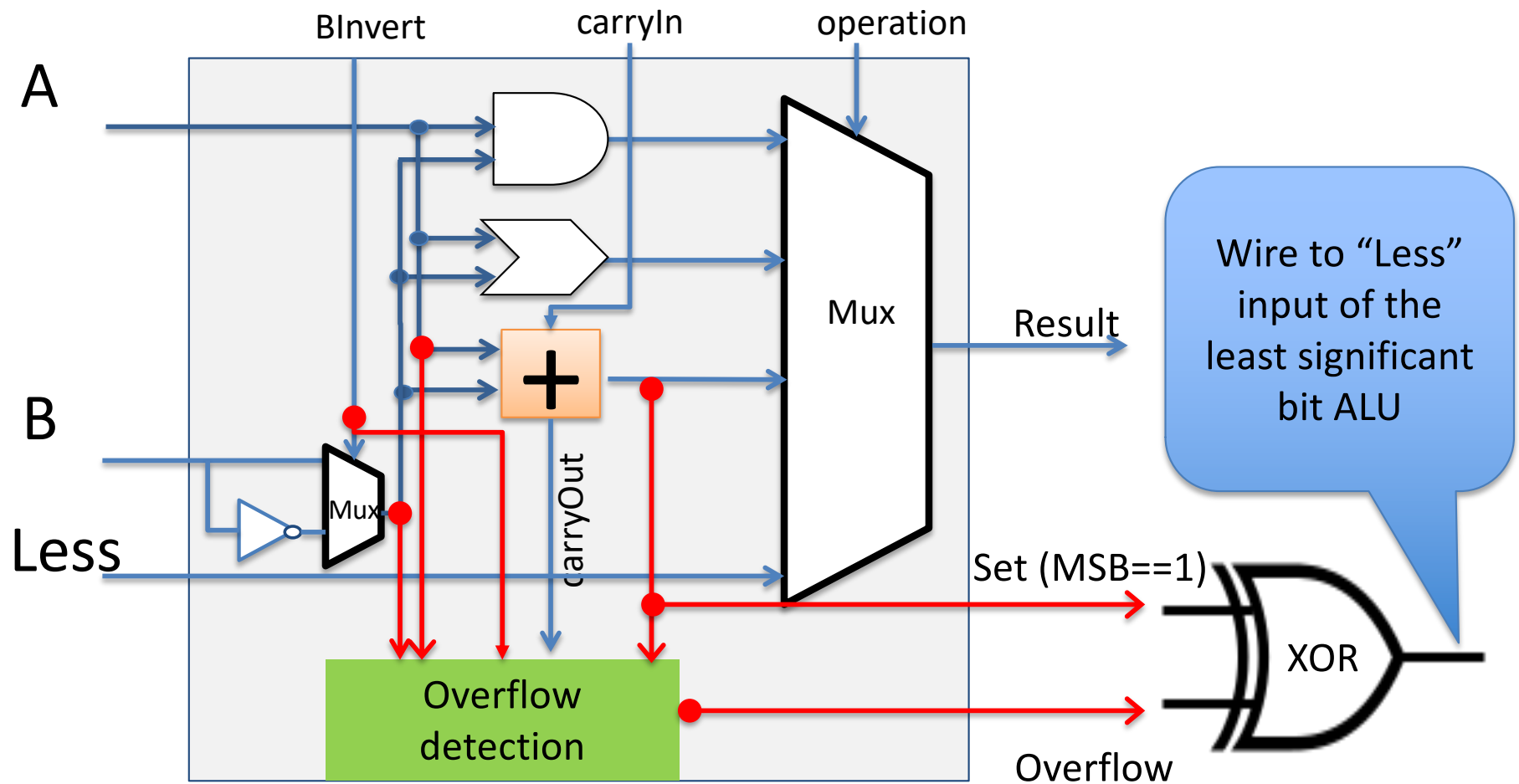- $A < B$ iff:
 - $(A-B)$ is negative (MSB is 1)
 - $(A-B)$ overflowed
 - But not both



Downside of ripple carry?

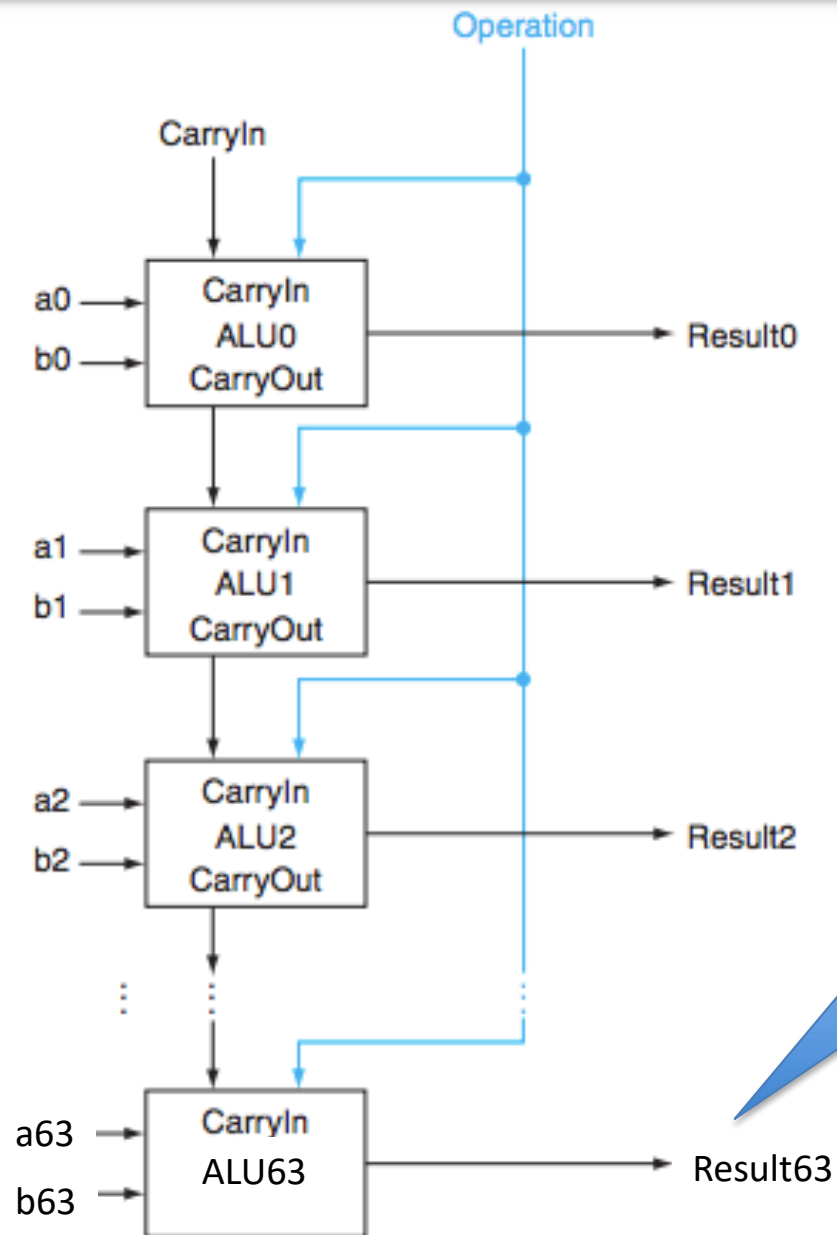


Must wait for sequential evaluation of all 64 1-bit adders

In search of faster adder

- Ripple carry:
 - Delay: 64, Gate count: $64 * c$
- Brute-force (truth table->PLA)
 - Delay: 2, Gate count: $O(2^{64+64})$
- Clever designs in between?
- Idea #1: (Carry lookahead) compute multiple carry-bits at a time

Faster adder: carry lookahead

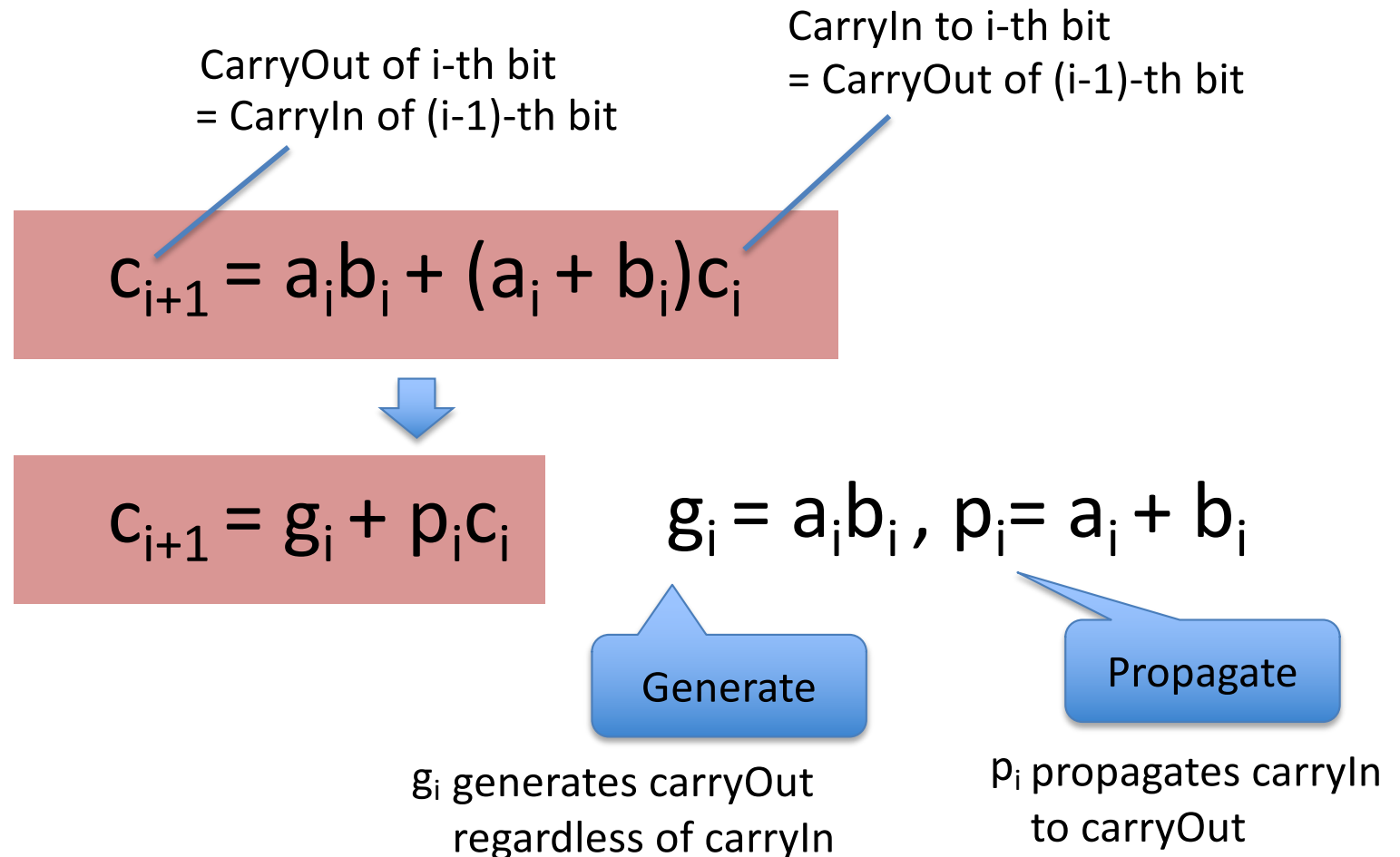- Idea #1: (Carry lookahead) compute multiple carry-bits at a time



Faster adder: carry lookahead

- Idea #1: (Carry lookahead) compute multiple carry-bits at a time

Computing all carry-bits of a 4-bit adder:

$$c1 = g0 + (p0 \cdot c0)$$

$$c2 = g1 + (p1 \cdot g0) + (p1 \cdot p0 \cdot c0)$$

$$c3 = g2 + (p2 \cdot g1) + (p2 \cdot p1 \cdot g0) + (p2 \cdot p1 \cdot p0 \cdot c0)$$

$$c4 = g3 + (p3 \cdot g2) + (p3 \cdot p2 \cdot g1) + (p3 \cdot p2 \cdot p1 \cdot g0) \\ + (p3 \cdot p2 \cdot p1 \cdot p0 \cdot c0)$$

Delay? 3

4-bit ripple carry
delay: $2 \cdot 4$

Faster adder: carry lookahead

- Idea #1: (Carry lookahead) compute multiple carry-bits at a time

Computing all result bits in a 4-bit adder:

$$s_i = \bar{c}_i \cdot a_i \cdot b_i + c_i \cdot \bar{a}_i \cdot b_i + c_i \cdot a_i \cdot \bar{b}_i, \quad i = 0, \dots, 3$$

Faster adder: carry lookahead

- Build a 16-bit adder with carry-ahead 4-bit adders

